

Roll No									
---------	--	--	--	--	--	--	--	--	--



# NATIONAL INSTITUTE OF TECHNOLOGY GOA

Farmagudi, Ponda, Goa, 403401

Programme Name: B.Tech./M.Tech./Ph.D.  
Mid Semester Examinations, October-2021

Course Name: MPMC

Date: 06/10/2021

Duration: 1 Hour 30 Minutes

Course Code:

Time: 2.00 to 3.30 PM

Max. Marks: 50

---

ANSWER ALL QUESTIONS

---

1. Design a 8085 memory interface circuit to map 32K X 8 bit memory. You are provided with a) 4K X 8 bit RAM memory -4 No.s and b) 8K X bit ROM memory – 01No. The starting address of ROM memory should be 0000H and the ending address of RAM memory should be FFFFH. Design all the intermediate logic circuits using logic gates. -20M
2. What is data path? Explain, with pictorial representations, the 8085 data path for the following instructions -10M
  - a) MOV A,M
  - b) LXI H,FFEF H
3. Design a 4 X 4 bit RAM memory using D Flip-flops, tri-state logic devices and decoders -10M
4. Write short notes on the following -10M
  - a) Computer a “Digital state machine”
  - b) Hardware and programming model of 8085.