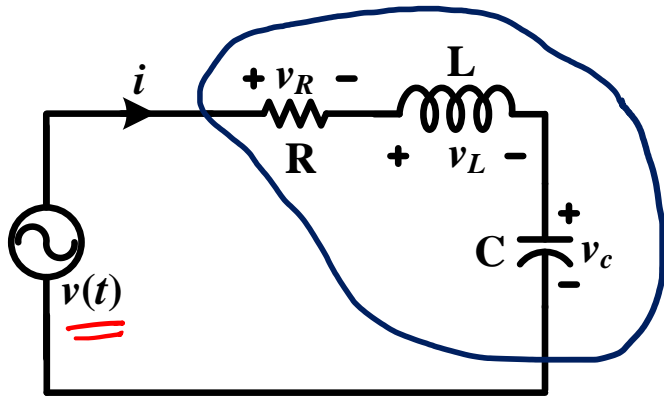


Expt5: Measurement of AC System quantities



✓ 1. Find load impedance.

✓ 1. Find load impedance.

2. Derive the expression of various responses.

3. Draw the phasor diagram of these responses.

4. Calculate various power components.

5. Calculate Power Factor.

6. Find the value of source frequency at which the power factor will be unity.

✓ $V(t) = 230\sqrt{2}\sin(100\pi t)$ feeds power to a load ($R = 10 \Omega$, $L = 1 \text{ mH}$, $C = 1 \text{ mF}$)

$$V(t) = 230\sqrt{2} \sin(100\pi t)$$

$$V_m \sin \omega t$$

↓

$\omega, f.$

$$\omega = 100\pi = 2\pi f$$

$$f = 50 \text{ Hz}$$

$$Z = R + j(X_L - X_C) \quad ; \quad X_L = 2\pi f L = 100\pi * 1 \times 10^{-3} = 0.314 \Omega$$

$$Z = 10 + j(0.314 - 3.185) \quad X_C = \frac{1}{2\pi f C} = \frac{1}{100\pi * 1 \times 10^{-3}} = 3.185 \Omega$$

$$= (10 - j2.869) \Omega$$


$$= \sqrt{10^2 + (-2.869)^2}$$

$$\tan^{-1}\left(\frac{-2.869}{10}\right)$$

$$\Rightarrow Z_{\text{Theo}} = 10.4 \angle -16.0^\circ \Omega$$

✓ 10.4 \angle -16.0
Simulation

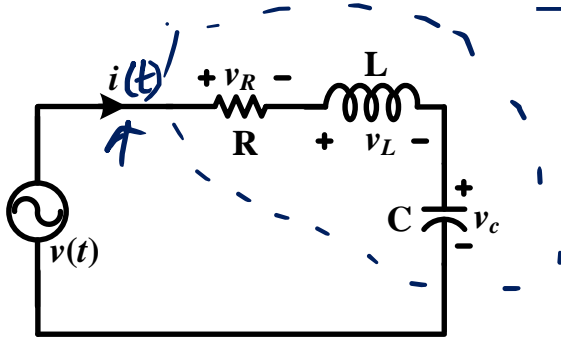Expt5: Measurement of AC System quantities



2. Derive the expression of various responses.

1. Find load impedance.

2. Derive the expression of various responses.


3. Draw the phasor diagram of these responses.

4. Calculate various power components.

5. Calculate Power Factor.

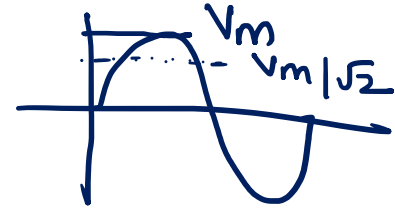6. Find the value of source frequency at which the power factor will be unity.

$$✓ V(t) = \underbrace{230\sqrt{2}}_{V_m} \sin(100\pi t) = 230 \angle 0^\circ \text{ RMS}$$




$$✓ Z(t) = \underline{10.4} \angle -16.01$$

$$✓ i(t) = \frac{V(t)}{Z(t)} = \frac{230 \angle 0^\circ}{10.4 \angle -16.01} = 22.11 \angle 16.01^\circ \text{ A} = 22.11\sqrt{2} \sin(100\pi t + 16.01)$$

$$✓ V_R = i(t) \cdot R = 22.11 \angle 16.01^\circ * 10 = 221.1 \angle 16.01^\circ \text{ Volts}$$

$$✓ V_L = i(t) \cdot X_L = 22.11 \angle 16.01^\circ * \underbrace{j(100\pi * 10^{-3})}_{0.314} = 22.11 \angle 16.01^\circ * 0.314 \angle 90^\circ = 6.946 \angle 106.01^\circ$$

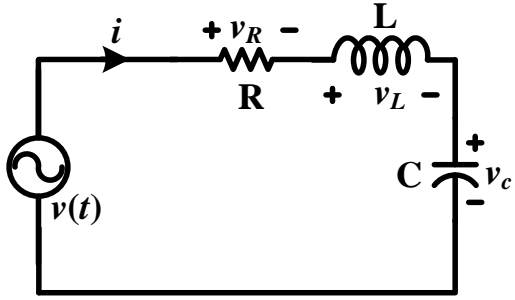Expt5: Measurement of AC System quantities



- ✓ 1. Find load impedance.
- ✓ 2. Derive the expression of various responses.
- ✓ 3. Draw the phasor diagram of these responses.
4. Calculate various power components.
5. Calculate Power Factor.
6. Find the value of source frequency at which the power factor will be unity.


2. Derive the expression of various responses.

$$V_c = i X_c = 22.11 \angle 16.01^\circ \times -j 3.185 = 22.11 \angle 16.01^\circ \times 3.185 \angle -90^\circ \\ = 70.42 \angle -74^\circ.$$

Simulation

$$V_{ms} = 325.22 \text{ (peak)} \\ i(t) = 31.26 \text{ (peak)}$$

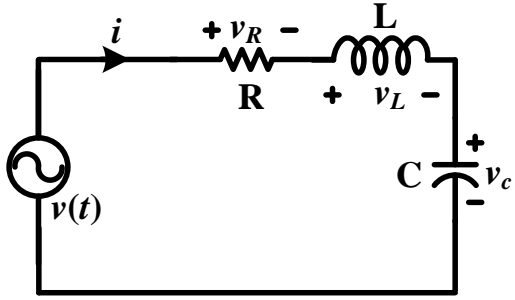Expt5: Measurement of AC System quantities



3. Draw the phasor diagram of these responses.

✓ $V(t) = 230 \angle 0^\circ$


✓ $i(t) = 22.11 \angle 16^\circ$

✓ $V_R = 221.1 \angle 16^\circ$


✓ $V_L = 6.94 \angle 106^\circ$

✓ $V_C = 70.42 \angle -74^\circ$

1. Find load impedance.
2. Derive the expression of various responses.
- ✓ 3. Draw the phasor diagram of these responses.
4. Calculate various power components.
5. Calculate Power Factor.
6. Find the value of source frequency at which the power factor will be unity.

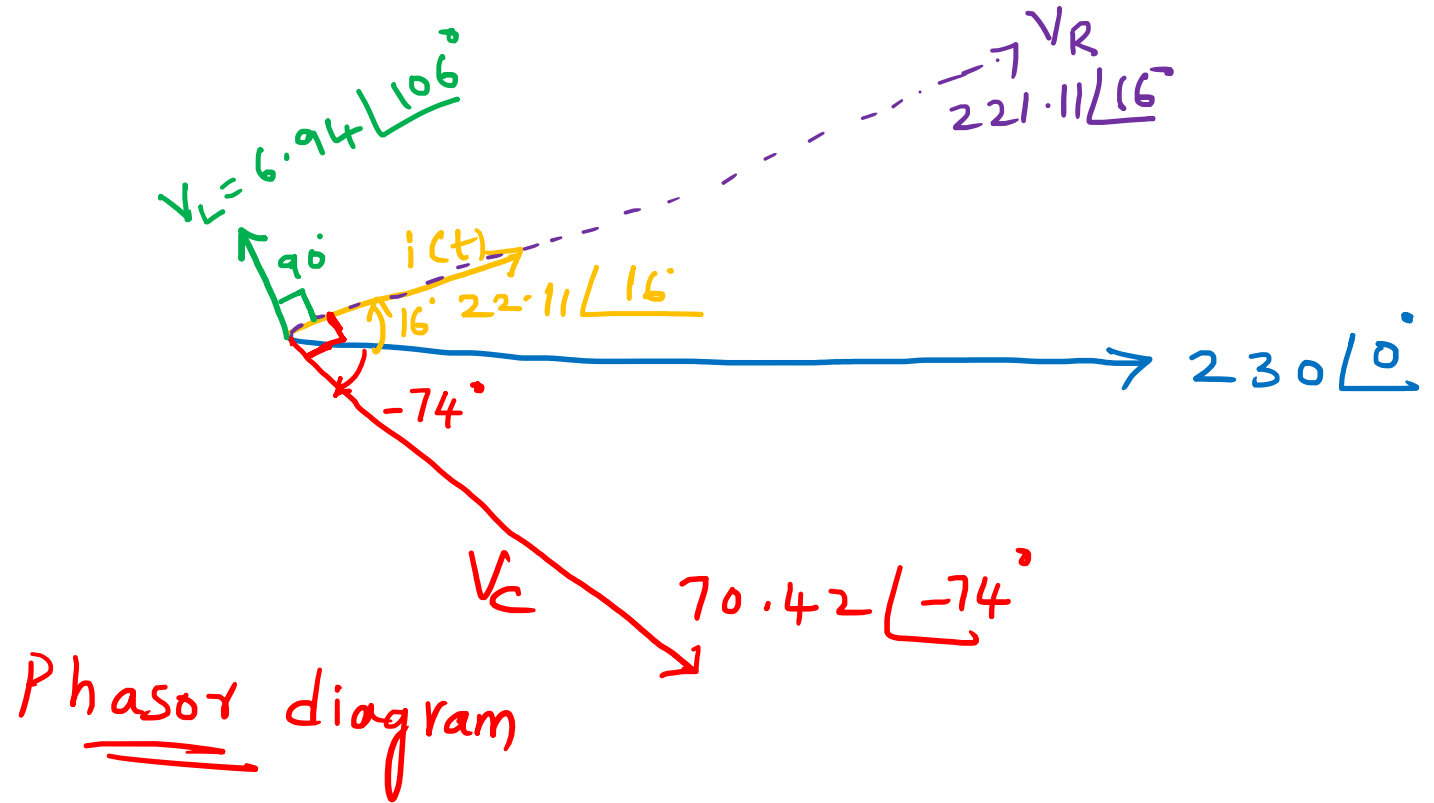

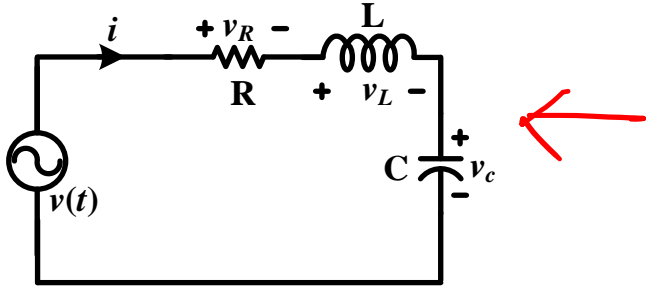Expt5: Measurement of AC System quantities




4. Calculate various power components.

Real power: 'P'

Reactive Power: 'Q'

Apparent Power: 'S'

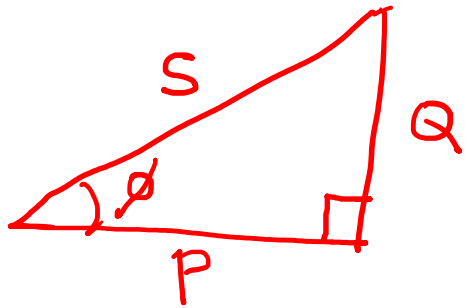

$$\cos \phi = \frac{P}{S} = \frac{R}{Z}$$

1. Find load impedance.
2. Derive the expression of various responses.
3. Draw the phasor diagram of these responses.
4. Calculate various power components.
5. Calculate Power Factor.
6. Find the value of source frequency at which the power factor will be unity.

$$S = V \cdot I^* = 230 \angle 0^\circ \times 22.11 \angle -16^\circ$$

$$\underline{\text{Sim}} (5082.43)_{\text{VA}} = 5085 \angle -16^\circ \leftarrow \phi$$

$$P = V I \cos \phi = S \cdot \cos \phi$$


$$= 5085 \cdot \cos(-16^\circ) \quad \text{Sim}$$

$$= 4888.3 \text{ W} \leftarrow (4885 \text{ W})$$

$$Q = V I \sin \phi = S \sin \phi$$

$$\text{Simulat} \rightarrow (-1401.8 \text{ VAR}) = -1401.7 \text{ VAR} \leftarrow$$

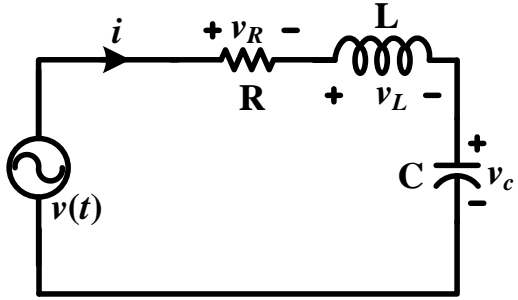Expt5: Measurement of AC System quantities




5. Calculate Power Factor.

1. Find load impedance.
2. Derive the expression of various responses.
3. Draw the phasor diagram of these responses.
4. Calculate various power components.
5. Calculate Power Factor.
6. Find the value of source frequency at which the power factor will be unity.

$$\cos \phi = \frac{P}{S} = \underline{0.9612} \leftarrow (\text{Simulation})$$

$$= \frac{4888.3}{5085} = 0.961317 (\text{Theoretically})$$

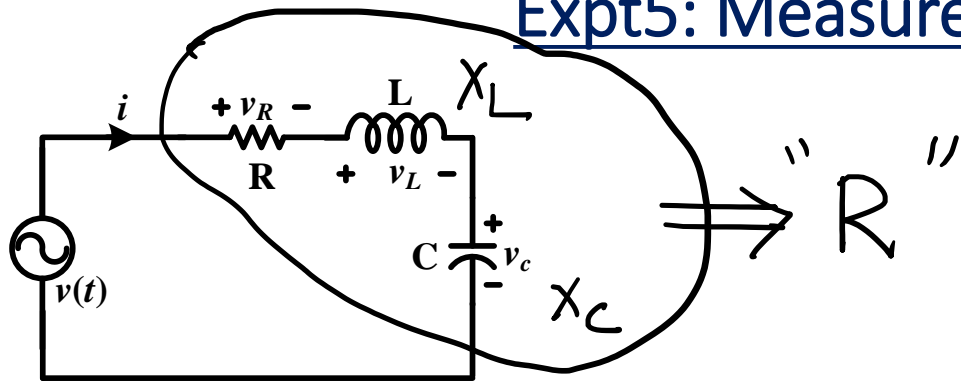Expt5: Measurement of AC System quantities



1. Find load impedance.
2. Derive the expression of various responses.
3. Draw the phasor diagram of these responses.
4. Calculate various power components.
5. Calculate Power Factor.
6. Find the value of source frequency at which the power factor will be unity.

6. Find the value of source frequency at which the power factor will be unity.

$$Z = R + j(X_L - X_C) \Rightarrow X_L - X_C = 0 \Rightarrow X_L = X_C$$

$$Z = R ; \text{Pf} \Rightarrow \text{Unity}$$

$$2\pi fL = \frac{1}{2\pi fC}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$


$$V(t) = 100 \pi = \omega \Rightarrow 2\pi f$$

$$\omega_{\text{new}}^{\text{UPF}} = 2\pi \cdot 159.23 = 1000 //$$

$$= 159.23 \text{ Hz}$$

Power factor angle ' ϕ ' from Simulation.

ϕ b/w V & I .

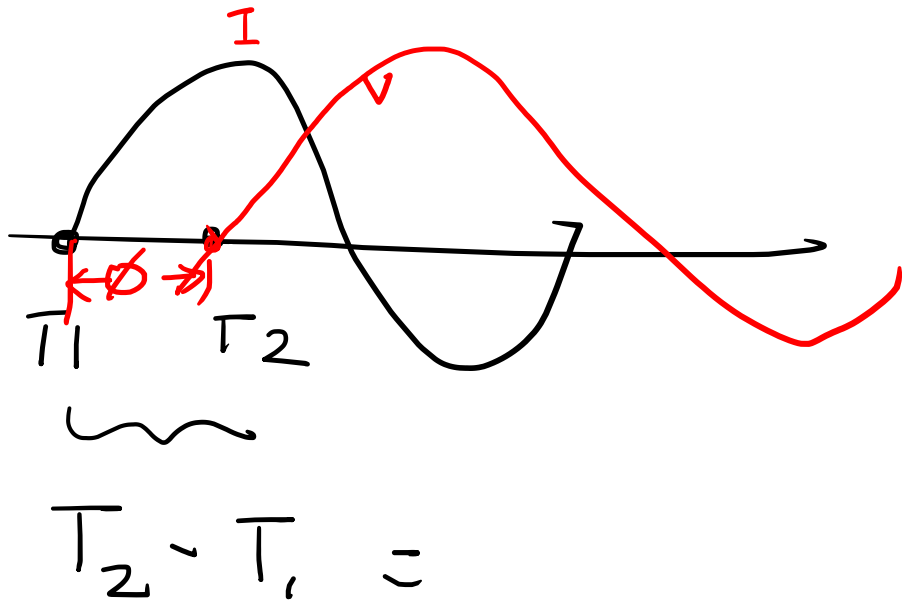

$$T_2 = 1.6 \text{ Sec}$$

$$T_1 = 1.5991$$

$$T_2 - T_1 = 0.0009 \text{ Sec}$$

$$\phi = \omega t = 100\pi \cdot (0.0009)$$

$$\phi_{\text{rad}} = 0.28269 \text{ rad} \times \frac{180}{\pi} \text{ Deg}$$
$$= 16.19^\circ //$$

Simulation \Rightarrow