Computer Organization and Architecture

Internal Organization of Memory Chips 2-d Address Decoding

Veena Thenkanidiyoor National Institute of Technology Goa




1

Recap

- Internal organization of memory chips
- · 1-d Address decoding
- · Motivation for 2-d address decoding

2-dimensional Address Decoding

 
- k-address line is divided into k/2 row address and k/2 column address
- Now, memory chip is considered as $2^{k/2} \times 2^{k/2}$ memory cell array
- Example: Design of 16 x 4 bit memory chip
 - Number of address lines: 4
 - Number of row address lines: 2
 - Number of column address line: 2





3


2-dimensional Address Decoding

 - k-address line is divided into k/2 row address and k/2 column address
- Now, memory chip is considered as $2^{k/2} \times 2^{k/2}$ memory cell array
- Example: Design of 16 x 4 bit memory chip
 - Number of address lines: 4
 - Number of row address lines: 2
 - Number of column address line: 2




 

 


 

′

 

Byte Addressable Memory

 

Word Byte Address Address 0 1 2 3 5 6 7 1 2 9 10 11 2^{k/4}-1 **2**^k**-3**

Little Endian

Big Endian

Example: Intel Processors


Motorola Processors


9


5


Static RAM Module


- Byte Addressable Memory
- Illustration:
 - Task: Design SRAM with capacity 8MB (2²³ B)
 - Requirements:
 - Memory organization depends on the word size and word size decides the width of the data bus
 - Let word size be 32 bit (4B)
 - Now, memory organization: 2M x 32 bit
 - Memory should be byte addressable
 - Let the organization of cell array to incorporate byte addressability be $1M \times 8$ bit
 - Organization include:
 - 2 rows of chips, each of size 1M x 8 bit
 - Each row contain 4 chips
 - Number of address lines: 23 (2²³ B)

 


 


 


 

 

 

 

 

Static RAM Module

4MB SRAM Module



19

19

Static RAM Module

- N: Capacity of SRAM
- n bits: Width of SRAM
- M: Capacity of one SRAM chip
- m bits: Width of SRAM chip
- Number of rows of memory chips: N/M
- Number of chips in a row: n/m
- According to the number of rows of memory chips and number of chips in a row, Chip Select (CS) logic is designed
- Higher order bits in address select a row of memory chips
- Lower order bits in address select a byte in a word
- Size line in CS logic indicates how many bytes in a word need to be selected

Reference

 Carl Hamacher, Zvonko Vranesic and Safwat Zaky, "Computer Organization", 5th Edition, Tata McGraw Hill, 2002

21

21

Thank You

22