
	<b>AGNEL INSTITUTE OF TECHNOLOGY AND DESIGN</b> <b>ASSAGAO, GOA-403 507</b>  <b>INTERNAL TEST – I</b>	
---	--	---

Sem – I

**Subject: BASIC ELECTRICAL AND ELECTRONICS ENGINEERING**

Max.Marks: 25


Date: 15-12-20



Duration: 1 hour

Read the following instructions for answering BEE IT I:

1. Students have to write the answers on plain paper. **Details like Name, Roll no, Subject and the students signature should be present on top corner of every page of answer sheet.**
2. After completing the paper, student has to scan and mail the answer paper in pdf format to [vh@aitdgoa.edu.in](mailto:vh@aitdgoa.edu.in) within 1hour i.e. between 12:00 pm-01:00 pm
3. The pdf file should be named as "**Students Roll No\_Subject\_IT1.pdf**"  
eg. "**20CO01\_BEE\_IT1.pdf**". Tools like Cam scanner can be used for scanning the answer sheet.

**Answer all Questions**

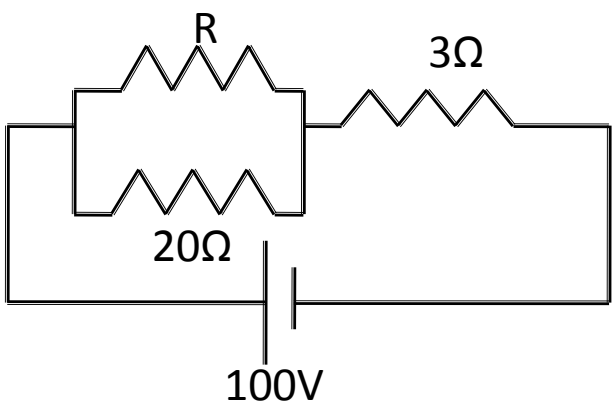1.	<p>A resistance R is connected in parallel in a circuit comprising of <math>20\Omega</math> and <math>3\Omega</math>. The total power dissipated in the circuit is 1000W and the applied voltage is 250V. Calculate R.</p> 	2	(CO1) (CO3)
----	---	---	----------------

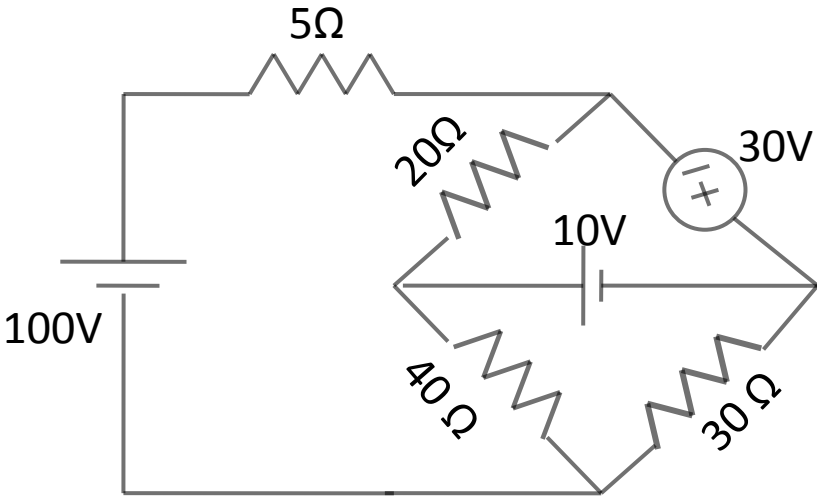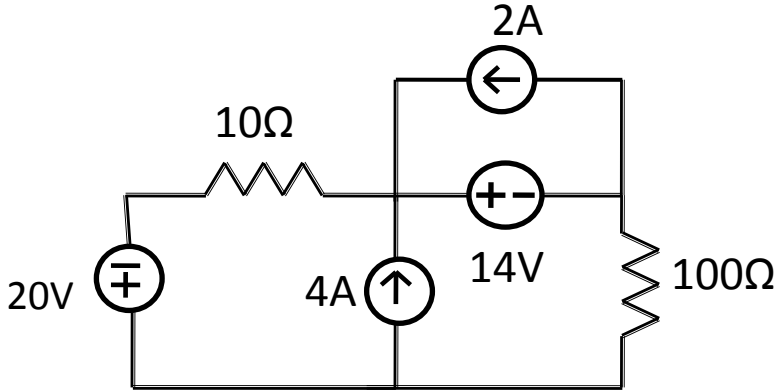2.	Find the loop currents using Mesh Analysis.	5	(CO1) (CO3)
			
3.	Find the current through the 100Ω using superposition theorem.	5	(CO1) (CO3)
			
4.	Explain PN junction diode characteristics with neat diagram. Differentiate between the avalanche and zener breakdown mechanism in a pn junction diode.	5	(CO1) (CO2)
5.	Obtain the expression for ripple factor and rectification efficiency of a full wave rectifier.	8	(CO1) (CO3)

Faculty Name

Vijaya Hadfadkar