


Network Theorems

R, L, C, V, I, Diode, BJT, op-amp.

Passive Element :- R, L, C

Active Element :- sources, amplifier

Linear Element : (R) : $V = IR$

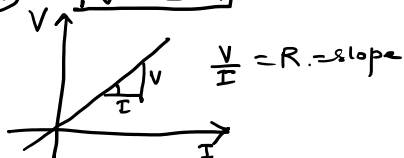

Inductance ; $V_L = L \frac{di}{dt}$; $V_L \propto \frac{di}{dt}$

Capacitor : $q = CV \Rightarrow \int i dt = CV$
 $i_c = C \frac{dV}{dt}$
 $i_c \propto \frac{dV}{dt}$


Linear Elements $\rightarrow R, L, C$.

Linearity Property

Additive property (adding)
 Homogeneity (scaling)

1 fruit - 10 Rs
 50 fruit $\rightarrow 50 \times 10$
 $\underline{\underline{= 500 Rs}}$


Additivity

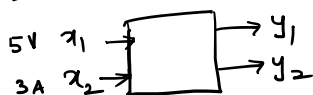

$$f(x_1 + x_2) = f(x_1) + f(x_2)$$

$$(x_1 + x_2) \rightarrow (y_1 + y_2)$$

Homogeneity

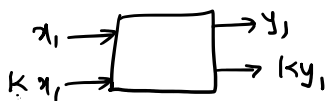

$$f(ax) = a f(x)$$

Linear ckt :



$V, I \rightarrow \text{forcing } f^n$

1) Linear Element :- A LE is a passive element that has a linear V-I relationship. R, L, C


2) Linear ckt :- A ckt composed entirely of

independent sources, linearly dependent sources
& Linear elements.



Independent sources

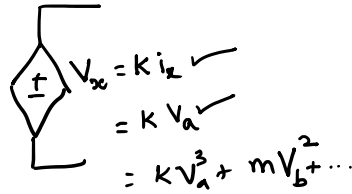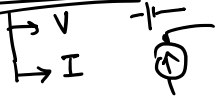

3) Bilateral Element :

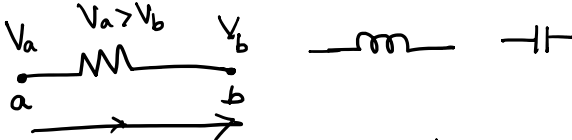

Non-Bilateral Element

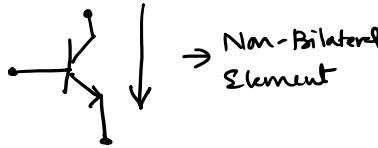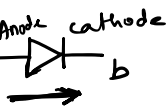


Superposition Principle

An electrical circuit satisfies superposition principle if it has a linear, bilateral, passive network. The voltage ^{across} or current through any resistor or source may be calculated by—
adding algebraically all the individual voltage or currents caused by separate independent sources acting alone, with all other independent voltage sources short circuited and current sources open circuited.


Network theorems


- Superposition theorem
- Thevenin's theorem
- Norton's theorem

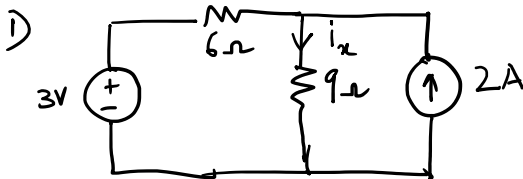- Max. power transfer
- Tellegen's
- Reciprocity thm



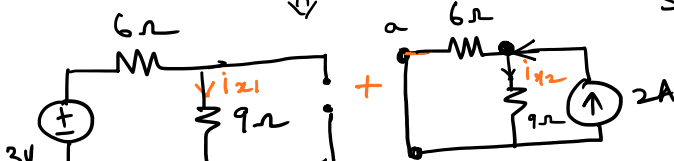Keep only one Independent source & nullify / kill all other independent sources




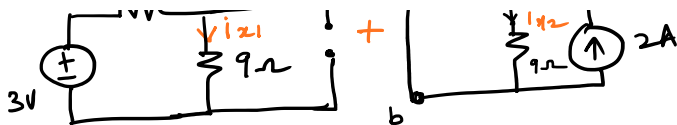

$$i_{x1} = \frac{3}{15} = 0.2A \quad \left| \quad i_{x2} = \frac{2 \times 6}{6+9} = \frac{4}{5} = 0.8A$$


$$i_x = i_{x1} + i_{x2} = 0.2 + 0.8 = 1A$$

②


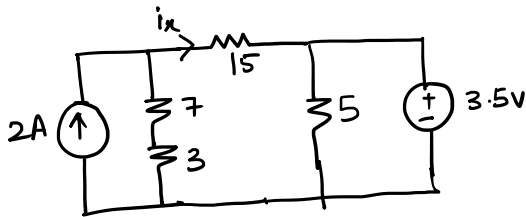


Superposition Theorem

$$i_x = ??$$

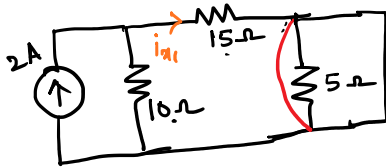

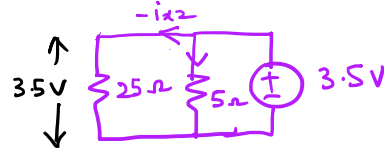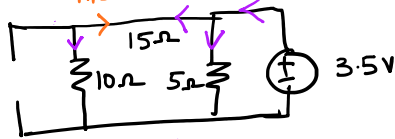
$$i_{x1} = \frac{2 \times 10}{(10+15)} = 0.8A$$




$$3.5V = -i_{x2} \cdot 25 \Rightarrow i_{x2} = -0.14A$$

$$i_x = i_{x1} + i_{x2} = 0.8 - 0.14 = 0.66A = 660mA$$

③

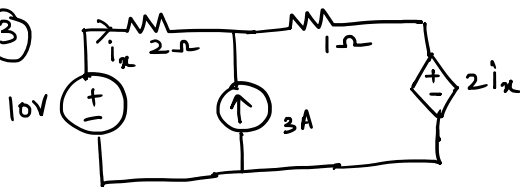


Compute i_x using Superposition Theorem

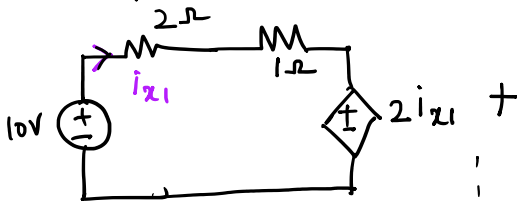


$$i_{x1} = \frac{(10 - 2i_{x1})}{3}$$

$$i_{x1} = 2A$$

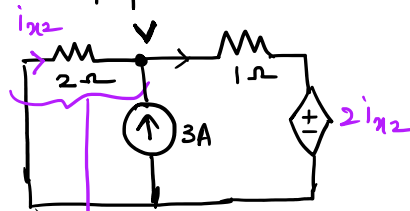


$$i_{x2} + 3 = \frac{(V - 2i_{x2})}{1}$$

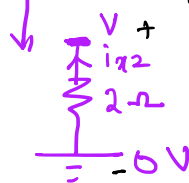

$$V = -2i_{x2}$$
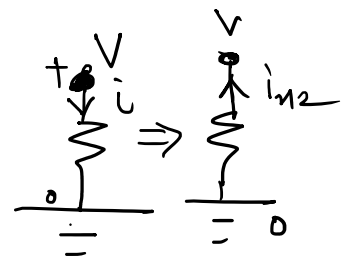
$$i_{x2} + 3 = (-2i_{x2} - 2i_{x2}) \Rightarrow i_{x2} = -0.6A$$




$$i_{x2} + 3 = (-2i_{x2} - 14)$$



$$i_{x2} = -3/5 = \underline{\underline{-0.6A}}$$

$$i_x = i_{x1} + i_{x2}$$
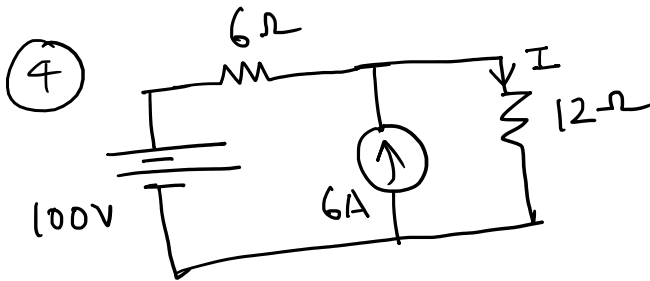
$$= 2 - 0.6 = \underline{\underline{1.4A}}$$



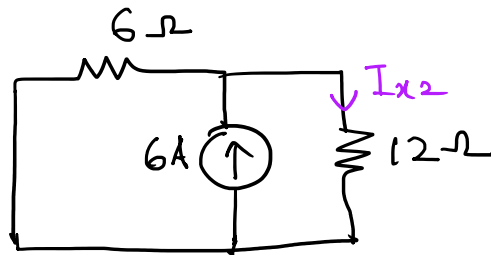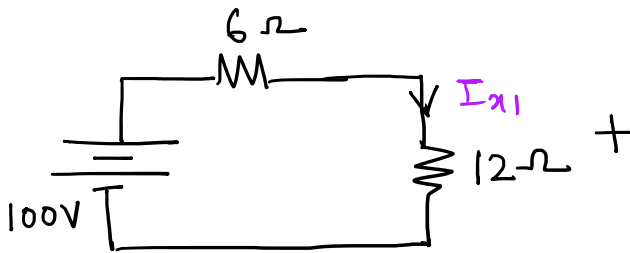Use Superposition theorem to find power absorbed by 12-Ω resistor



$$684.03W \checkmark$$

$$P_{loss} = I^2 \cdot R$$

$$= (I_{x1} + I_{x2})^2 \cdot 12 = (2 + 5.55)^2 \cdot 12 = 684.03W \checkmark$$

$$\left\{ \begin{array}{l} P_{loss \text{ in ck1}} \Rightarrow I_{x1}^2 \cdot (12) \\ P_{loss \text{ in ck2}} \Rightarrow I_{x2}^2 \cdot (12) \end{array} \right\} X$$