

Basic Electrical Science

Assignment - 02

1. For a R-L series circuit excited by a DC source of 60 V, considering $R = 30\ \Omega$ and $L = 15\text{ H}$; Plot the following graphs in an **.xls sheet**:

- Series current through the circuit wrt time (in sec)
- Voltage across Inductor wrt time (in sec)
- Voltage across Resistor wrt time (in sec)
- Power absorbed by the Inductor wrt time (in sec)
- Power dissipated by the Resistor wrt time (in sec)

Consider the time variation from 0 - 10 Sec in steps of 0.25 sec.

Check the results for time constant ' τ ' = 0.25, 0.5, 1, 2

2. For a R-C series circuit excited by a DC source of 60 V, considering $R = 30\ \Omega$ and $C = 0.1\text{ F}$; Plot the following graphs in an **.xls sheet**:

- Series current through the circuit wrt time (in sec)
- Voltage across Capacitor wrt time (in sec)
- Voltage across Resistor wrt time (in sec)
- Power absorbed by the Capacitor wrt time (in sec)
- Power dissipated by the Resistor wrt time (in sec)

Consider the time variation from 0 - 15 Sec in steps of 0.25 sec.

Check the results for time constant ' τ ' = 2, 3, 4, 5

3. For a R-L series circuit excited by a DC source, compute
- the time at which Power across the Inductor is maximum
 - Value of maximum P across the Inductor
4. For a R-C series circuit excited by a DC source, compute
- the time at which Power across the Capacitor is maximum
 - Value of maximum P across the Capacitor

Date of Assignment Submission: 12th February 2021