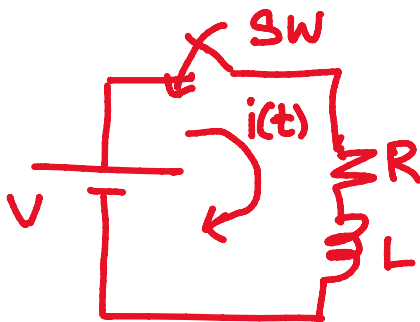


Problems on Transient Analysis with DC Excitation

RL Response Due to DC Excitation



Time Constant

$$\tau = L/R$$

$$i(t) = \frac{V}{R} \left[1 - e^{-\frac{Rt}{L}} \right] \quad \text{V, R, L, t}$$


$$V_L = V e^{-\frac{Rt}{L}}$$

$$V_R = V \left[1 - e^{-\frac{Rt}{L}} \right]$$

$$P_R = \frac{V^2}{R} \left[1 - 2e^{-\frac{Rt}{L}} + e^{-\frac{2Rt}{L}} \right]$$

$$P_L = \frac{V^2}{R} \left[e^{-\frac{Rt}{L}} - e^{-\frac{2Rt}{L}} \right]$$

RC Response Due to DC Excitation

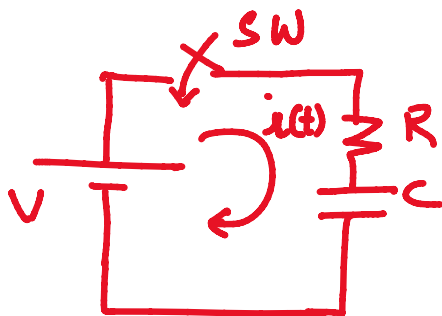

Time Constant

$$\tau = RC$$

$$i(t) = \frac{V}{R} \left[e^{-\frac{t}{RC}} \right]$$


$$V_R = V \left[e^{-\frac{t}{RC}} \right]$$

$$V_C = V \left[1 - e^{-\frac{t}{RC}} \right]$$

$$P_R = \frac{V^2}{R} \left[e^{-\frac{2t}{RC}} \right]$$

$$P_C = \frac{V^2}{R} \left[e^{-\frac{t}{RC}} - e^{-\frac{2t}{RC}} \right]$$

RL

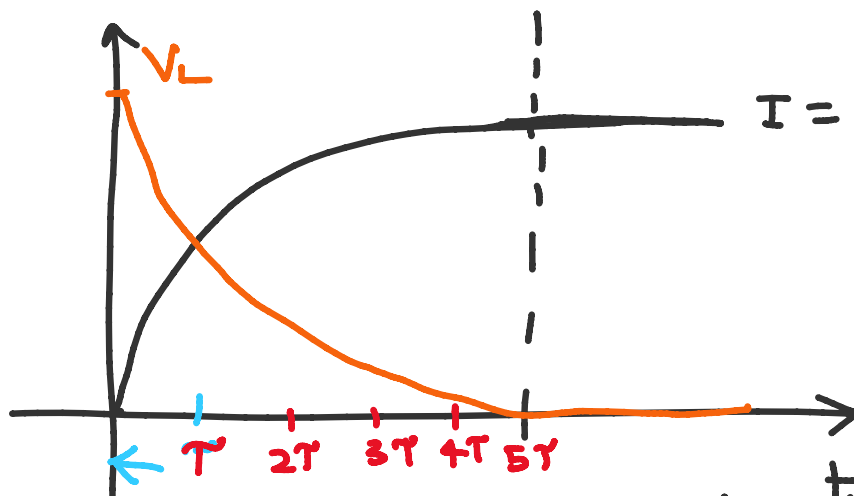


$$I = \frac{V}{R} \quad \left| \quad \frac{V}{R} \left[1 - e^{-Rt/L} \right] \right.$$

$$\tau = L/R$$

$$1\tau = 37\%$$

$$1\tau = 63\%$$

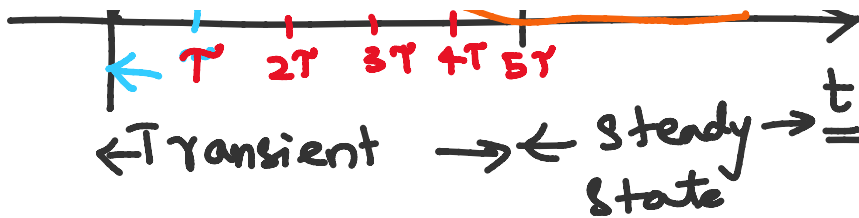


$$1T = 63\%$$

1. A series R-L Circuit with $R = 30 \Omega$ and $L = 15 \text{ H}$ is connected to a constant voltage of 60 V applied at $t = 0+$. Determine the current $i(t)$, Voltage across resistor and inductor at $t = 10 \text{ sec}$

$$i(t) = \frac{V}{R} \left[1 - e^{-Rt/L} \right]$$

$$= \frac{60}{30} \left[1 - e^{-\left(\frac{30 \times t}{15}\right)} \right]$$

$$= 2 \left[1 - e^{-2t} \right]$$

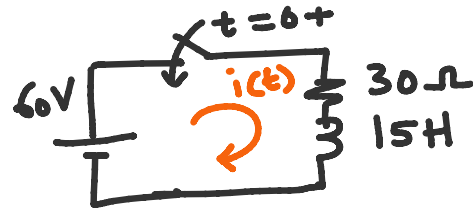

\therefore at $t = 10 \text{ sec}$ $i(t) = 2 \text{ A}$

at $t = 10 \text{ msec}$; $i(t) = 0.039 \text{ A}$

$$e^{-2(10)} = 2.06 \times 10^{-9}$$

$$\frac{e^{-2(10 \times 10^{-3})}}{e^{-0.02}} = e^{-0.02}$$

$$= 0.98019$$

$$V_R = V \left[1 - e^{-\frac{Rt}{L}} \right]; \tau = \frac{L}{R}$$

$$= V \left[1 - e^{-t/\tau} \right] = \frac{15}{30} = 0.5$$

$$= 60 \left[1 - e^{-t/0.5} \right] = 60 \left[1 - e^{-2t} \right]$$

@ $t = 10 \text{ sec}$; $V_R = 60 \text{ V}$

@ $t = 10 \text{ msec}$; $V_R = 0.597 \text{ V}$.

$$V_L: V e^{-Rt/L} \Rightarrow V e^{-t/\tau} = 60 e^{-2t}$$


$$V_L : V e^{-t/\tau} \Rightarrow V e^{-\infty} = 0 \text{ V}$$

$$\textcircled{a} t = 10 \text{ sec} ; V_L = 0 \text{ V}$$

$$\textcircled{a} t = 10 \text{ msec} ; V_L = 58.811 \text{ V}$$

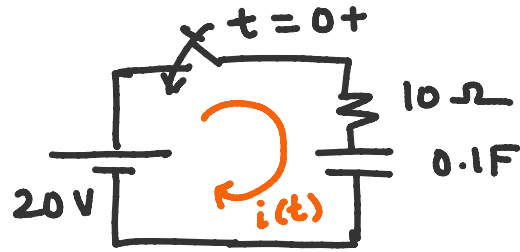2. A series R-C Circuit with $R = 10 \Omega$ and $C = 0.1 \text{ F}$ is connected to a constant voltage source of 20V applied across it at $t = 0+$. Determine the current $i(t)$, Voltage across resistor and capacitor at $t = 20 \text{ sec}$ and 20 msec .

$$\begin{aligned} i(t) &= \frac{V}{R} \left[e^{-t/RC} \right] \\ &= \frac{V}{R} \left[e^{-t/\tau} \right] \\ &= \frac{20}{10} \left[e^{-t/1} \right] \\ &= 2(e^{-t}) \end{aligned}$$



$$\begin{aligned} \tau &= RC = 10 \times 0.1 \\ &= 1 \end{aligned}$$

$$\textcircled{a} t = 20 \text{ sec} ; i(t) = 0$$

$$\textcircled{a} t = 20 \text{ msec} ; i(t) = 1.96 \text{ A}$$

$$\begin{aligned} V_R &= V e^{-t/RC} \\ &= 20 e^{-t} \end{aligned}$$

$$\textcircled{a} t = 20 \text{ sec} ; V_R = 0$$

$$\textcircled{a} t = 20 \text{ ms} ; V_R = 19.604 \text{ V}$$

$$V_C = V \left[1 - e^{-t/\tau} \right]$$



$$= 20 \left[1 - e^{-t/20} \right]$$

a) $t = 20 \text{ sec}$; $V_L = 20 \text{ V}$.

a) $t = 20 \text{ msec}$; $V_L = 0.396 \text{ V}$

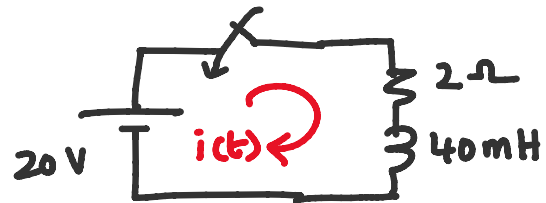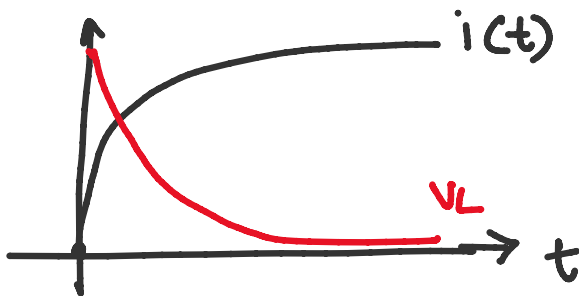3. A Coil having an inductance of 40 mH and a resistance of 2Ω is connected together to form an LR series circuit, with 20 V DC source across it.

- Determine the final steady state current in the circuit
- What will be the time constant of the RL series circuit
- What will be the transient time of the RL series circuit
- What will be the value of induced emf across the inductor after 10 ms
- What will be the value of the circuit current 1 time constant after the switch is closed.



$$\tau = \frac{L}{R} = \frac{40}{2} = 20 \text{ msec}$$

(a) Current $i(t) = \frac{V}{R} \left[1 - e^{-t/\tau} \right]$

Steady State Current = 10 A .

(b) $\tau = \frac{L}{R} = \frac{40}{2} = 20 \text{ msec}$

(c) Transient time = 5τ

$$= 5 \times 20 \text{ msec}$$

$$= 5 \times 20 \text{ msec}$$

$$= 100 \text{ msec}$$

$$(d) \quad V_L = V e^{-\frac{Rt}{L}} = 20 e^{-t/\tau}$$

after 10 msec $\cdot \frac{10 \times 10^{-3}}{20 \times 10^{-3}}$

$$V_L = 20 e^{-\frac{10 \times 10^{-3}}{20 \times 10^{-3}}} = 20 \times 0.6065 = 12.13 \text{ V}$$

(e) after 1 time constant $t = \tau$.

$$i(t) = \frac{20}{2} (1 - e^{-t/\tau}) = 10 (1 - 0.368) = 6.32 \text{ A}$$

