

Total No. of Printed Pages: 4

**F. E. (Semester-II) (Revised Course 2007-08)**  
**EXAMINATION SEPTEMBER 2020**  
**Basic Electronic Engineering**

[Duration : Two Hours]

[Total Marks : 60]

**Instructions:**

- 1) Answer THREE FULL QUESTIONS with ONE QUESTION from ANY THREE MODULES.
- 2) Draw neat, labeled diagram wherever necessary.
- 3) All symbols and abbreviations carry their usual meaning.
- 4) Make suitable assumptions when necessary.

**MODULE- I**

- Q1. a) What is meant by dynamic resistance of a semiconductor diode? Explain how it is determined graphically. (6 marks)
- b) Explain the piecewise-linear equivalent circuit for a silicon diode using relevant diagrams. (4 marks)
- c) Differentiate between transition and diffusion capacitance in a p-n junction diode. (4 marks)
- d) i) Determine the current  $I$  for the network of fig 1 (6 marks)

 


Fig 1

- ii) Determine  $V_O$  and  $I_D$  for the following network (Fig 2)

 


Fig 2

What is the minimum value of  $E$  required in the above circuit for current to flow in the circuit?

- Q2. a) For the Zener diode voltage-regulator circuit in Fig 3, determine  $V_L$ ,  $V_R$ ,  $I_z$  and  $P_z$ . (5 marks)  
Comment on the safety of operation of the Zener diode.

 


Fig 3

- b) What are diode clamping networks? For the following network, Determine the output waveform. (5 marks)

 


Fig 4

- c) With a neat circuit diagram and waveforms, explain the working of a half-wave rectifier, and derive the expression for  $V_{rms}$  and  $V_{dc}$ . (8 marks)
- d) Explain Peak Inverse Voltage (PIV) for a rectifier circuit. (2 marks)

## MODULE -II

- Q3. a) Explain the amplifying action of a bipolar junction transistor with a neat diagram. (5 marks)
- b) Explain the cut-off region for a common-emitter BJT transistor configuration. Obtain the relationship between  $I_{CEO}$  and  $I_{CBO}$ . (5 marks)
- c) For the following network of Fig 5, determine (6 marks)
- i)  $I_B$ , ii)  $I_C$ , iii)  $V_{CE}$  iv)  $V_C$  v)  $V_E$  vi)  $V_B$

 


Fig 5: Emitter bias network

d) Explain the working of a BJT as a switch. (4 marks)

Q4. a) With neat diagrams explain the input and output characteristics of a BJT in the common-base configuration. Highlight the three basic regions of interest. (7 marks)

b) Obtain the relationship between  $\alpha$  and  $\beta$  for a BJT. (3 marks)

c) Explain the limits of operation for a BJT and define the linear region of operation on the output characteristics. (7 marks)

d) Define a.c. current gain for a BJT. Calculate the same, if a change in  $I_B$  from  $100\mu A$  to  $150\mu A$  causes a change in  $I_C$  from  $5mA$  to  $7.5mA$ . (3 marks)

### MODULE- III

Q5. a) Explain in detail the construction and operation of an n-channel JFET. Explain what you mean by pinch-off. (8 marks)


b) Using the shorthand method, obtain the transfer curve for a JFET and a sketch the transfer curve for a p-channel JFET with  $I_{DSS} = 4mA$  and  $V_P = 3V$ . (6 marks)

c) Explain the construction and basic operation of a n-channel depletion type MOSFET. (6 marks)

Q6. a) With neat circuit diagrams explain the analysis of a FET fixed-bias circuit and obtain expressions for various voltages. (6 marks)

b) With a neat diagram explain the construction and working of CMOS. What are the advantages of CMOS? (6 marks)

 - c) For the n-channel depletion-type MOSFET of Fig 6, determine: (8 marks)
- $I_{DQ}$  and  $V_{GSQ}$
  - $V_{DS}$



#### MODULE-IV

- Q7. a) Explain the grown-junction and diffusion methods to manufacture discrete transistors with neat diagrams. (6 marks)
- b) What is meant by the term monolithic integrated circuit (IC). List the steps in the fabrication of a monolithic IC wafer. (6 marks)
- c) Explain the op-amp operation in brief, with single-ended input. (4 marks)
- d) Explain the concept of “feedback” and draw the block diagram of a basic feedback amplifier. (4 marks)
- Q8. a) Explain the working of a transmissive type field –effect LCD with a diagram. (6 marks)
- b) Draw the general block diagram of a cathode-ray oscilloscope (CRO) and explain the operation. (6 marks)
- c) Write short notes on (any two): (8 marks)
- Photo-conductive cells
  - IR emitters and applications
  - Silicon controlled rectifier (SCR)