



## SEM 2 – 5 (RC 07-08)

### F.E. Semester – II (RC 07-08) Examination, May/June 2018 BASIC ELECTRONICS ENGINEERING

Duration : 3 Hours

Total Marks : 100

- Instructions :** 1) Attempt **any five** questions choosing at least **one** question from **each** Module.  
2) Draw **neat**, labelled diagrams **wherever** necessary.  
3) **All** symbols and abbreviations carry their usual meaning.  
4) Make **suitable** assumptions when **necessary**.

#### MODULE – I

1. a) Draw and explain the V-I characteristics of a silicon diode. Highlight the Forward-bias, Reverse-bias and No-bias regions on the graph. 6  
b) Why are silicon diodes preferred over germanium diodes ? 2  
c) Distinguish between avalanche and zener breakdown mechanisms in a semiconductor diode. 6  
d) With neat diagrams explain the piecewise-linear and simplified equivalent circuits for a diode. 6
2. a) i) Determine the value of  $V_0$  for the following network (Fig. 1)

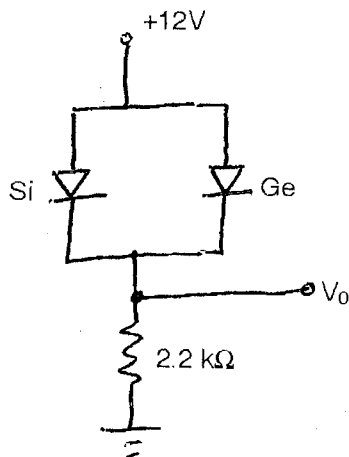


Fig. 1

P.T.O.



ii) Determine  $I_D$ ,  $V_{D_2}$  and  $V_0$  for the following circuit (Fig. 2).

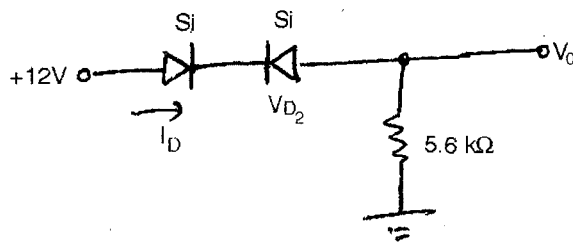


Fig. 2

b) With a neat circuit diagram and waveforms explain the working of a full-wave bridge rectifier. Also draw the output waveform if a C-filter is connected across the load.

c) For the following networks (Fig. 3) determine  $V_0$  and draw the output waveform.

i)

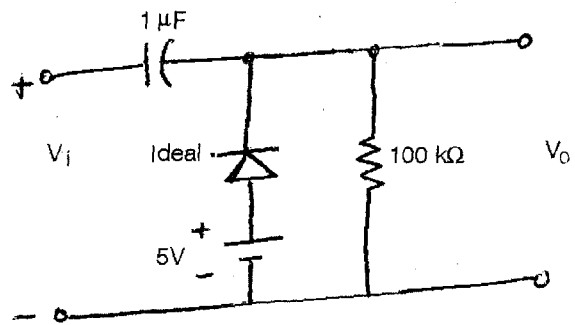
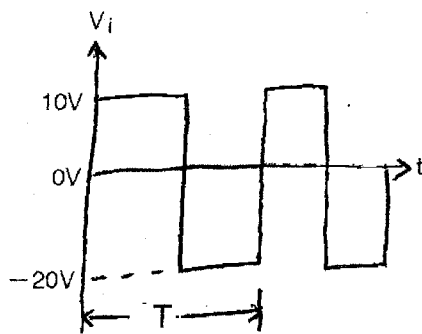


Fig. 3(a)

ii)


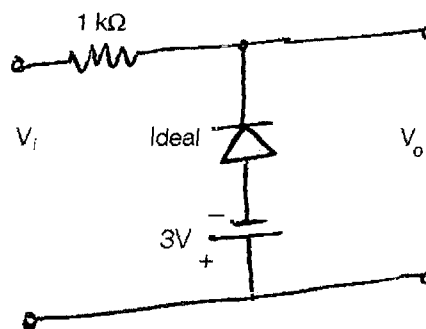


Fig. 3(b)

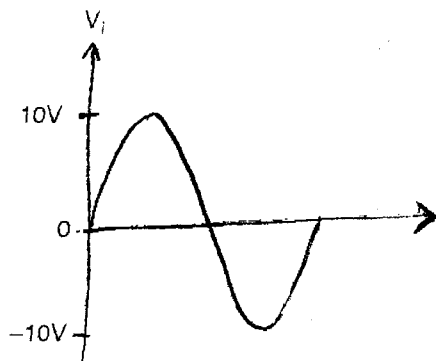

MODULE – II

3. a) Why is a transistor called a 'transistor' ? With a neat circuit-diagram, explain the amplifying action of a bipolar junction transistor.

6

b) With neat diagrams explain the common-emitter configuration of a bipolar junction transistor. Draw the collector and base characteristics (input and output characteristics). Explain the active, cut-off and saturation regions and highlight them on the graph.

8

c) Determine the following for the network given in Fig. 4

a)  $I_{BQ}$  and  $I_{CQ}$

b)  $V_{CEQ}$

c)  $V_B$  and  $V_C$

d)  $V_{BC}$

6

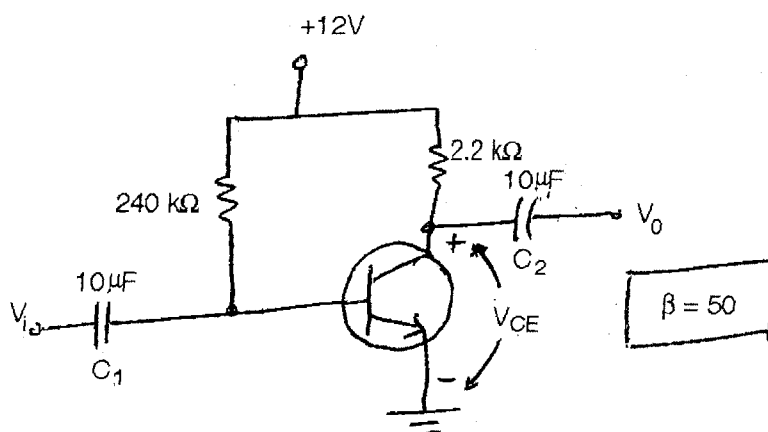


Fig. 4 Fixed bias circuit



4. a) Draw the circuit diagram of an emitter-stabilized biased BJT circuit and hence derive the expressions for  $I_B$ ,  $R_i$ ,  $V_{CE}$ ,  $V_C$  and  $V_B$ . What is the advantage of this circuit over fixed bias circuit ? 7
- b) Determine the dc bias voltage  $V_{CE}$  and the current  $I_C$  for the configuration shown in Fig. 5. 8

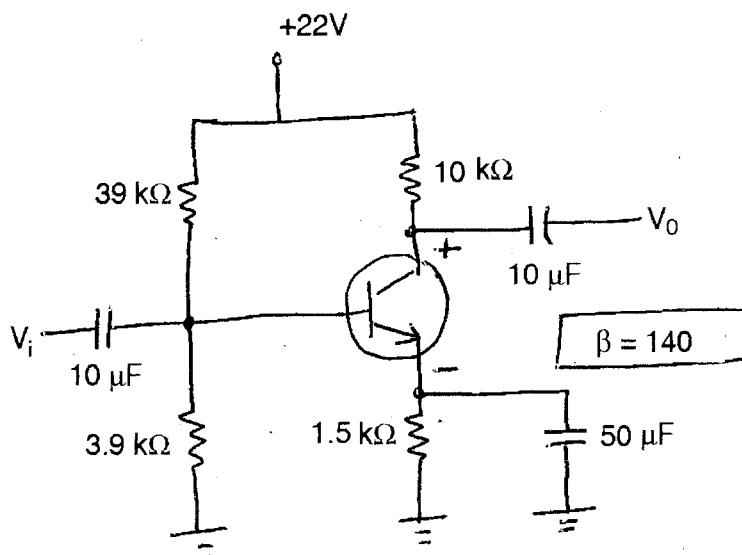


Fig. 5

- c) Explain the design and operation of a transistor as a switch. 5


### MODULE – III

5. a) Explain in detail the construction and operation of an n-channel JFET. Explain what you mean by pinch-off in a JFET. 8
- b) Using the shorthand method, obtain the transfer curve for a JFET and sketch the transfer curve for a p-channel JFET with  $I_{DSS} = 4 \text{ mA}$  and  $V_p = 3 \text{ V}$ . 6
- c) Explain the construction and basic operation of a n-channel depletion type MOSFET. 6
6. a) With neat circuit diagrams explain the analysis of a FET fixed bias circuit and obtain expressions for various voltages. 6
- b) With a neat diagram explain the construction and working of CMOS. What are the advantages of CMOS ? 6



c) Determine  $I_{DQ}$ ,  $V_{GSQ}$  and  $V_{DS}$  for the network in Fig. 6.

8

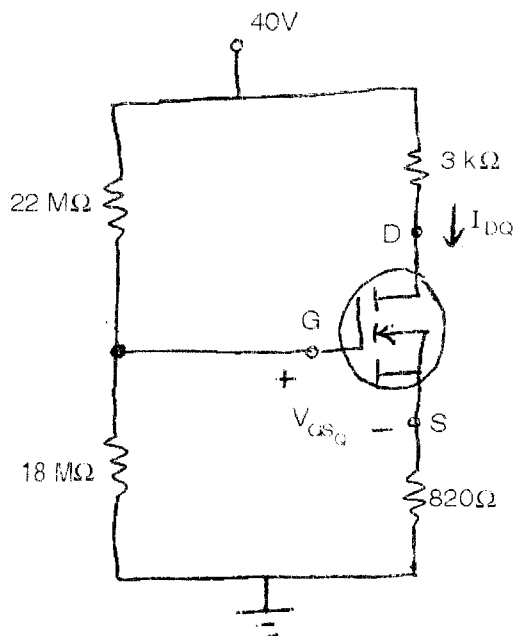

2N4351 (enhancement type)

$V_{GS}(\text{Th}) = 5\text{V}$

$I_D(\text{on}) = 3\text{ mA}$

at  $V_{GS}(\text{on}) = 10\text{V}$

Fig. 6

#### MODULE – IV

7. a) Explain the grown-junction and diffusion methods to manufacture discrete transistors, with neat diagrams. 6
- b) What is meant by the term monolithic integrated circuit ? List the steps in the fabrication of a monolithic IC wafer ? 6
- c) Explain the op-amp operation in brief with differential input. 4
- d) Explain the concept of “feedback” and draw the block diagram of a basic feedback amplifier. 4
8. a) Explain the working of a reflective type field-effect LCD with a diagram. 6
- b) Draw the general block diagram of a cathode ray oscilloscope (CRO) and explain the operation of a CRO. 6
- c) Write short notes on (**any two**) : 8
  - i) IR emitters and applications
  - ii) Solar cells
  - iii) Silicon Controlled Rectifier (SCR).