



Roll No.

National Institute of Technology Goa

Programme Name: B.Tech., I Sem

END Semester Examinations, April 2021

Course Name: Basic Electrical Science

Date: 07th April 2021

Duration: 3 Hours


Course Code: EE151

Time: 9:30 AM – 12:30 PM


Max. Marks: 100 Marks

ANSWER ALL THE QUESTIONS TO THE POINT

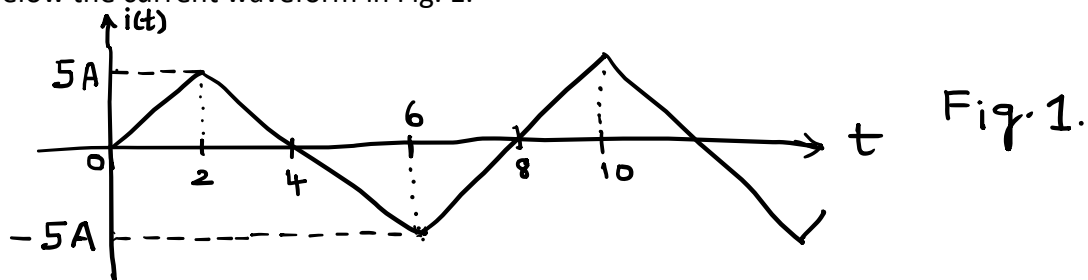
1. Find below the current waveform in Fig. 1.



- Write the equation of voltage that produces this current through an inductor of 2 H [3 M]
 - Represent graphically the Voltage expression obtained in 1(a) [2 M]
 - Find the equation of Charge driving this current [3 M]
 - Represent graphically the Charge expression obtained in 1(c) [2 M]
2. For the coupled network shown in the Fig. 2, write the three loop equations using Kirchhoff's Voltage law for the **given current directions**. [3+2+3=8 M]

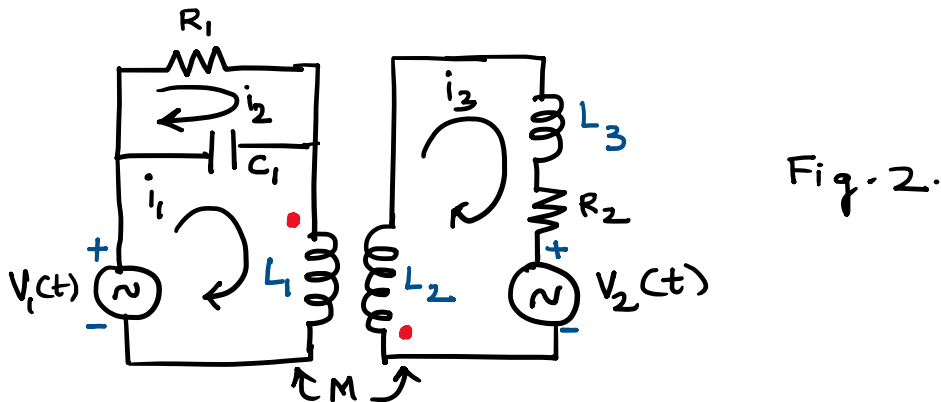

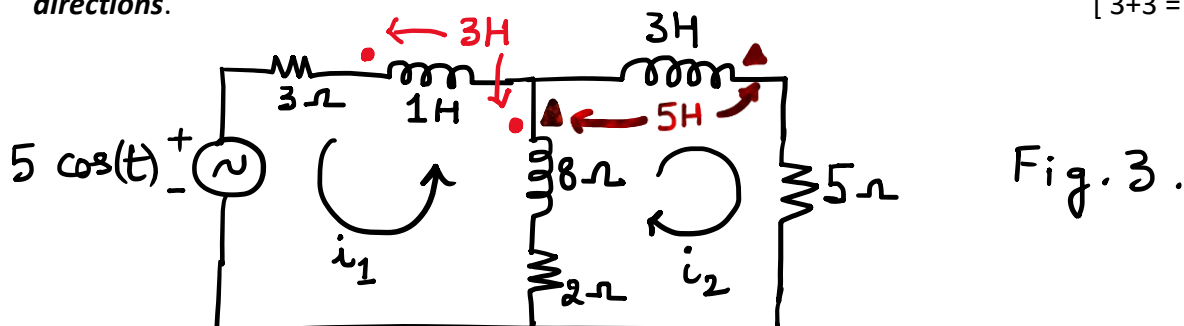3. For the magnetically coupled network given in Fig.3. formulate the loop equations for the **given current directions**. [3+3=6 M]



4. In the network given in Fig. 4., all the sources are time invariant. Determine the value of i_2 . [12 M]

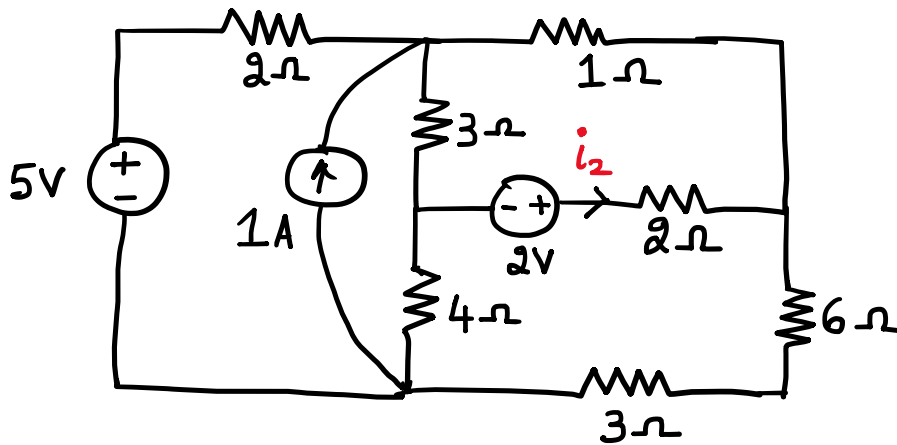


Fig. 4.

5. For the expression: $V(t) = 12 \cos(\omega t - \pi/6)$ Volts
- Represent graphically $V(t)$ wrt ωt (rad) [3 M]
 - Represent graphically $V(t)$ wrt t (sec) [2 M]
 - Represent $V(t)$ in Polar form [1 M]
 - If $V(t)$ is applied across an ideal Capacitor of $C = 3$ mF, compute $i(t)$ through the capacitor. [2 M]
 - Do the Phasor representation of $V(t)$ and $i(t)$ [2 M]
6. Consider the circuits given in Fig. 5 and Fig. 6, write the output Voltages $V_o(t)$. Consider the forward bias drop across the diode 'D' to be 1.1 V for each of the cases. [5 + 5 = 10 M]

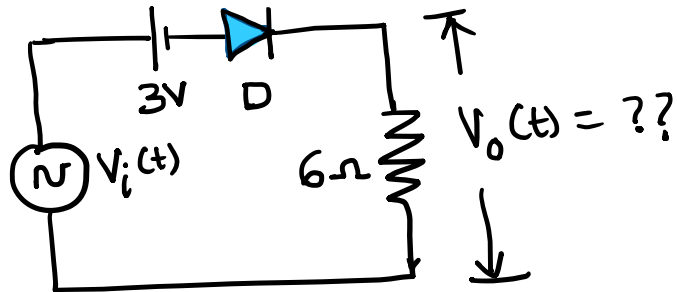
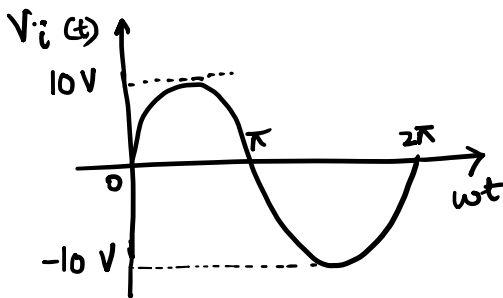


Fig. 5


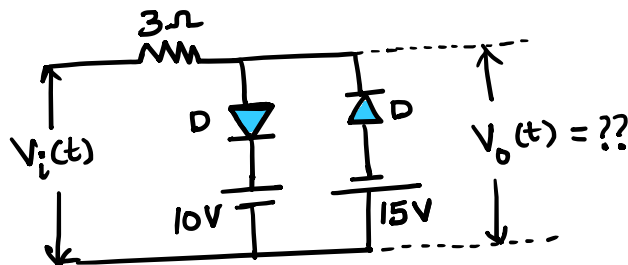
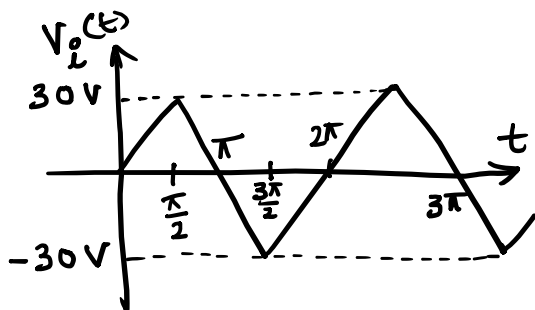



Fig. 6

7. A fullwave P-N junction diode rectifier is connected across a load resistor of $1500\ \Omega$. Assuming ideal diode characteristics with a forward diode resistance $0\ \Omega$ and an AC voltage of $V_i(t) = 40 \sin(\omega t)$ Volts, 50 Hz applied across the primary side of the center-tapped transformer, Calculate the below:

[2+1.5+1.5+2+2+2 = 11M]

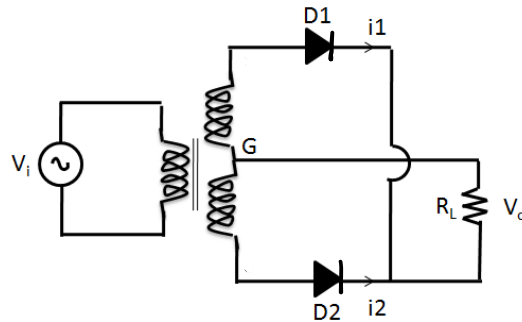

- Draw the output Voltage and Current waveforms across the Load
 - Average value of load current
 - RMS value of load current
 - Rectifier efficiency
 - Ripple factor
 - Draw the Peak Inverse Voltages across D1 and D2.
8. Using 1s complement, compute $(52)_{10} - (98)_{10}$ [3M]
9. Using 2s complement, compute $(74)_{10} - (09)_{10}$ [3M]
10. For the below Gate interconnection, write the Boolean expression for 'F' and its truth table. [2+3 M]

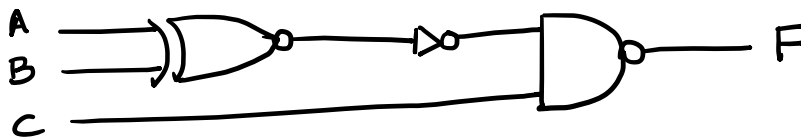

11. Consider $F = A\bar{B} + \bar{A}BC$. Prove that $F \cdot \bar{F} = 0$ and $F + \bar{F} = 1$ for the given function 'F'. [5 M]
12. Reduce $F = \bar{A}B(\bar{D} + \bar{C}D) + B(A + \bar{A}CD)$ to minimum number of literals. [4M]
13. Consider $F = AB(\bar{C}D + C\bar{D}) + \bar{A} \cdot \bar{B}(\bar{C} + D) \cdot (\bar{D} + C)$
- Find the complement of 'F' [4 M]
 - Realize 'F' using logic gates [4 M]
14. You plan to procure a very high processing speed Laptop with a good storage space. Discuss on the RAM, SRAM, DRAM and Hard disk capabilities you must look for, with proper justification and example. [5 M]
