

## **Chapter-4 Assignment**

**Due Date: 27<sup>th</sup> March 2021**

### **1. Solve the below**

- i.  $(658.825)_{10} = ( \quad )_8$
- ii.  $(532.65)_{10} = ( \quad )_{16} = ( \quad )_2$
- iii.  $(5372.65)_5 = ( \quad )_{10} = ( \quad )_2$
- iv.  $(9398.65)_{16} = ( \quad )_8 = ( \quad )_2$
- v.  $(11000110.010101)_2 = ( \quad )_{10} = ( \quad )_8 = ( \quad )_{16}$
- vi.  $(ABCDE.FGH)_{16} = ( \quad )_{10} = ( \quad )_8$

### **2. Perform the below using 1s complement and 2s complement independently**

- a.  $(56)_{10} - (34)_{10}$
- b.  $(85)_{10} - (105)_{10}$
- c.  $(65)_{10} - (155)_{10}$

### **3. Write the Graphical Symbol, Boolean Expression's function, Switch representation and Truth Table for the following Gates**





- a. OR
- b. AND
- c. NOT
- d. NOR
- e. NAND
- f. Exclusive-OR
- g. Exclusive-NOR

### **4. Consider three inputs to a GATE and represent the following symbolically**

- a. 3 input NOR Gate
- b. 3 input NAND Gate
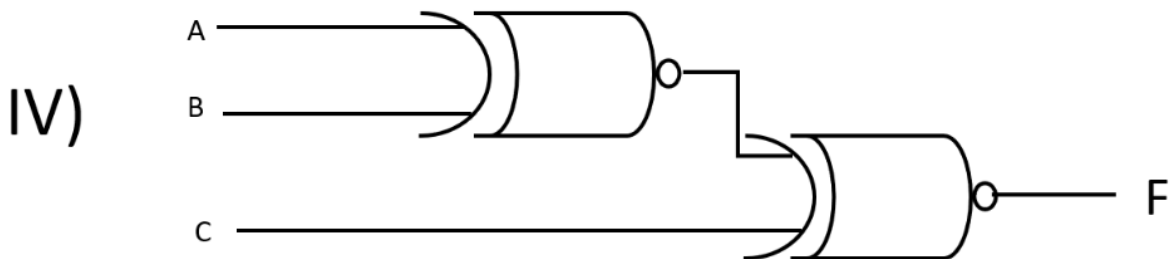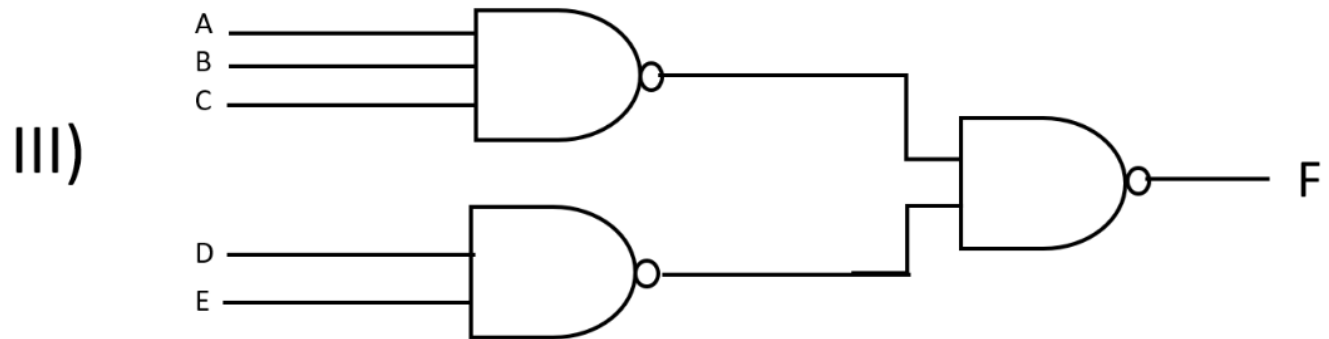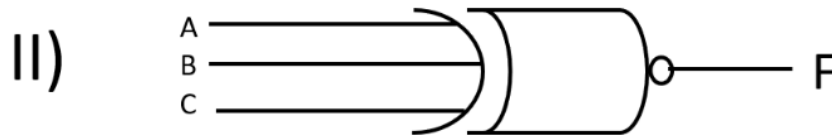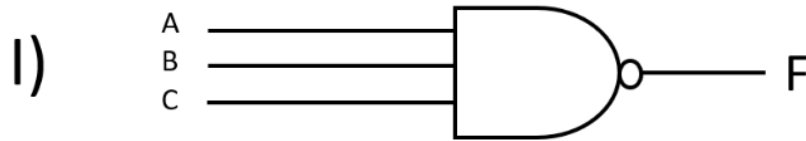
## 5. For the following Gate inter Connections

- Write the output Boolean expression (i.e., F)
- Truth Table of 'F'



**6. Simplify the following Boolean Expressions to a minimum number of literals (ie., variables)**

- a.  $AB + A + AB$  (Ans: A)
- b.  $\overline{\overline{AB} + ABC + A(B + A\overline{B})}$  (Ans: 0)
- c.  $ABC + AB\overline{C} + \overline{B}A$  (Ans: AB+BC)
- d.  $\overline{\overline{AB} + ABC + A(B + A\overline{B})}$  (Ans: 0)
- e.  $\overline{A} + AB + A\overline{C} + \overline{A}\overline{B}\overline{C}$  (Ans:  $\overline{A} + B + \overline{C}$ )
- f.  $(A+B)(A+\overline{B})$  (Ans: A)
- g.  $\overline{A}B(\overline{D} + \overline{C}D) + B(A + \overline{A}CD)$  (Ans: B)
- h.  $(\overline{A}+C)(\overline{A}++\overline{C})(A + B + \overline{C}D)$  (Ans:  $\overline{A}(B+\overline{C}D)$ )

**7. Realize the below Boolean expressions using logic gates**

- a.  $F = AB + C\overline{D} + \overline{B}C$
- b.  $F = (A+B)(\overline{C} + \overline{B})(\overline{D} + D + E)$

**8. Given the following Boolean Function**

$$F = A\overline{B}C + \overline{A}\overline{B}C + \overline{D}AB + D\overline{A}B + DAB$$

- a. Obtain the truth table for the given function 'F'
- b. Draw the logic gate diagram using Boolean expression
- c. Simplify the function to a minimum number of literals using Boolean algebra (Ans:  $\overline{B}C + B(D + A)$ )
- d. Obtain the truth table using the simplified function obtained from 8(c)

**9. Write in brief about the following Memory Elements:**

SRAM, DRAM, ROM, PROM, EPROM, EEPROM.

**Reference Book for Digital Electronics: 'Digital Design' by Morris Mano**

\*\*\*\*\*