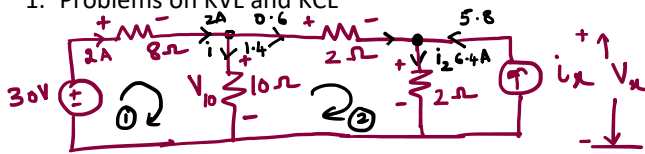


## Topics

1. Problems on KVL and KCL
2. Series-Parallel Voltage and Current Sources
3. Voltage and Current Division rule
4. Source Transformation

### 1. Problems on KVL and KCL




$$\text{Loop 1} \quad 30 - 16 - V_{10} = 0 \Rightarrow V_{10} = 14V$$

$$i = \frac{V_{10}}{10} = \frac{14}{10} = 1.4A$$

$$\text{Loop 2} \quad 14 - 1.2 - 2i_2 = 0 \Rightarrow i_2 = 6.4A \checkmark$$
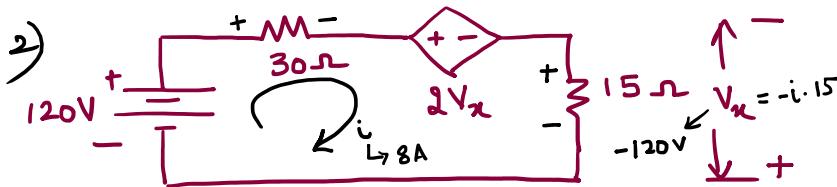
$$i_x = 5.8A; V_x = 6.4 \times 2 = 12.8V \checkmark$$



Compute the power absorbed in each element of the ckt shown;  $i, V_x$


$$120 - 30i - 2V_x + V_x = 0$$

$$V_x = -15i$$

$$120 - 30i - V_x = 0 \Rightarrow 120 - 30i + 15i = 0$$

$$\boxed{V_x = -15 \times 8 = -120V}$$

$$\boxed{i = 8A}$$

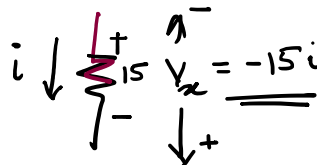

### Power Absorbed

$$\text{Battery: } P = VI = 120 \times 8 = 960W$$

$$\text{① } \begin{array}{c} \uparrow + \\ \downarrow - \end{array} \quad P_{\text{absorbed}} = -960W$$

$$\text{② } \begin{array}{c} 30\Omega \\ + \quad - \\ \rightarrow RA \end{array} \quad P_{\text{absorbed}} = I^2 R = 8^2 \times 30 = 1920W$$



②  $\frac{50W}{8A} \rightarrow 8A$   $P_{\text{absorbed}} = I R$   
 $= 8^2 \times 30 = 1920W$

③  $10V$   $8V$   $2V_x$   $i = 8A$   $P_{\text{absorbed}} = 2(-120)8$   
 $= -1920W$


④  $15\Omega$   $8A$   $P_{\text{absorbed}} = 8^2 \times 15$   
 $= \underline{\underline{960W}}$

## Series-Parallel Source Connections


### Voltage Source

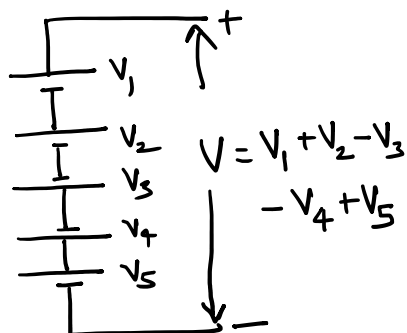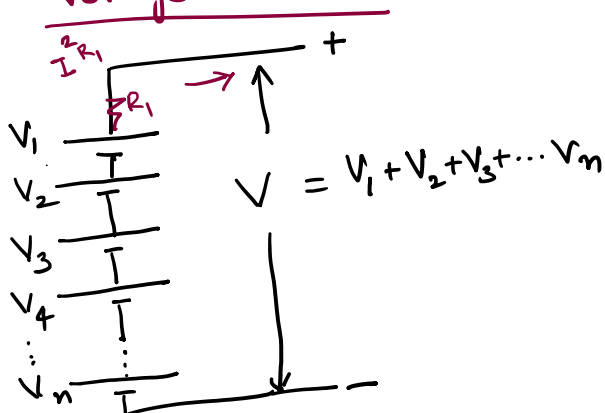


### Parallel Connection.

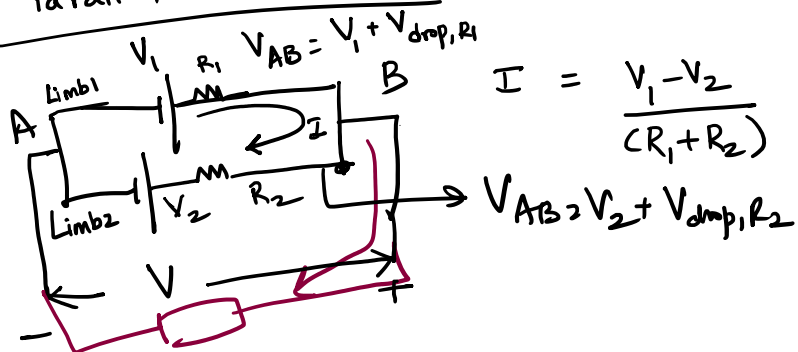


### Current Source

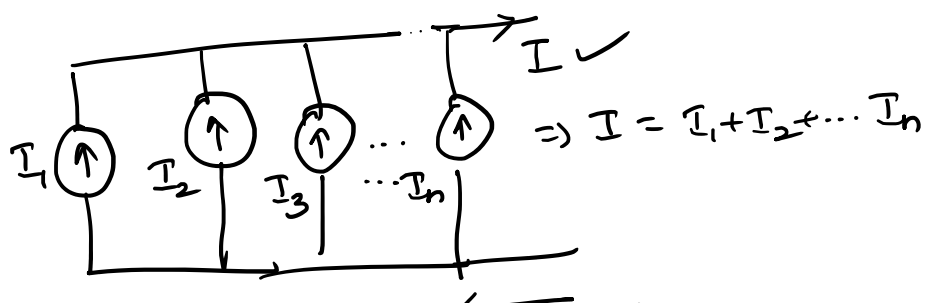

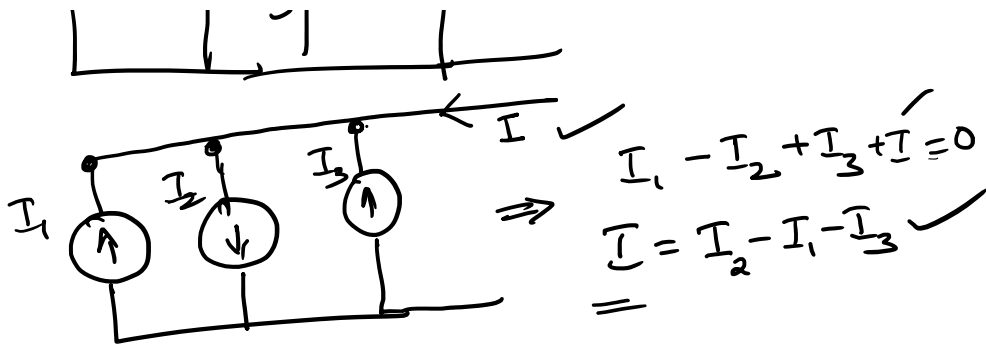


## Voltage Division Rule

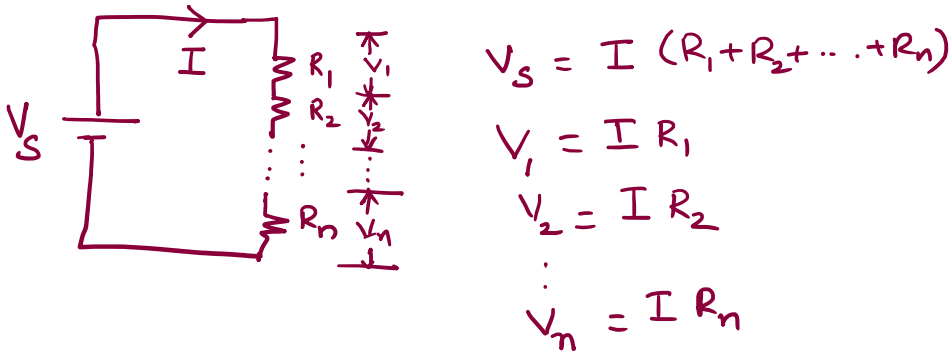

$$V_1 = I R_1 = \frac{V_S \cdot R_1}{(R_1 + R_2 + \dots + R_n)}$$

$$V_2 = I R_2 = \frac{V_S \cdot R_2}{(\sum R)}$$

## Current Division Rule

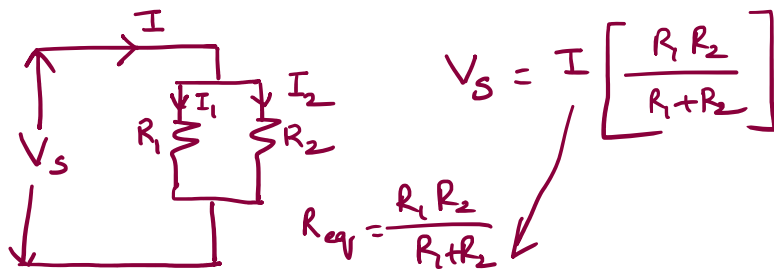


$$I_1 = \frac{V_S}{R_1} = \frac{I}{R_1} \left[ \frac{R_1 R_2}{R_1 + R_2} \right] =$$

$$I_1 = \frac{I \cdot R_2}{(R_1 + R_2)} ; I_2 = \frac{I \cdot R_1}{(R_1 + R_2)}$$

$$(R_1 + R_2)$$





$$(R_1 + R_2)$$

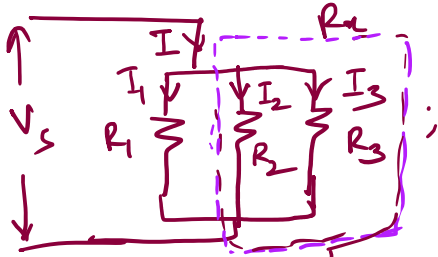


$$I_1 = \frac{I R_2}{(R_1 + R_2)}$$

$$\left( \frac{R_2 R_3}{R_2 + R_3} \right) \Rightarrow R_x$$

## SOURCE TRANSFORMATION.

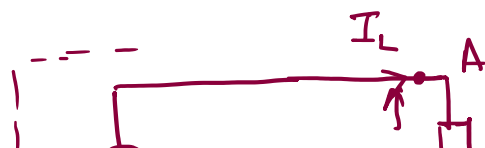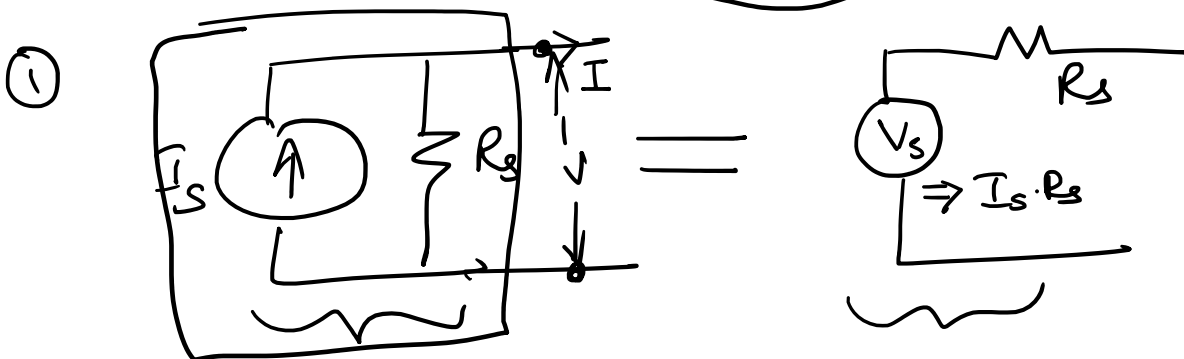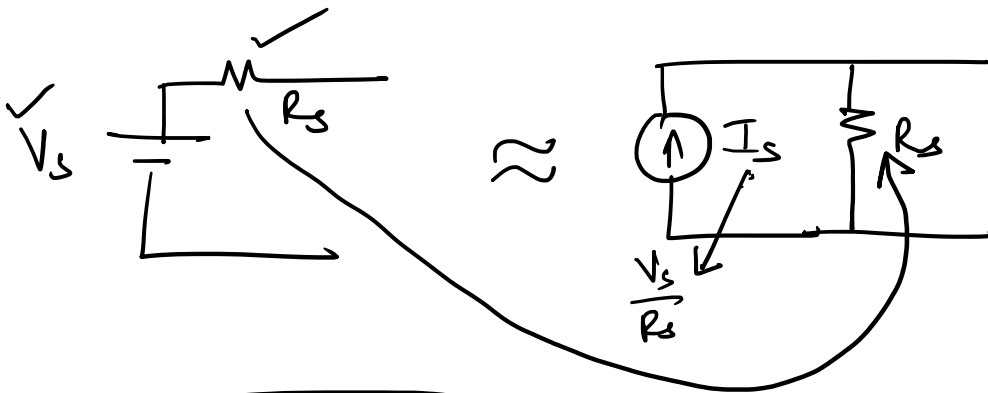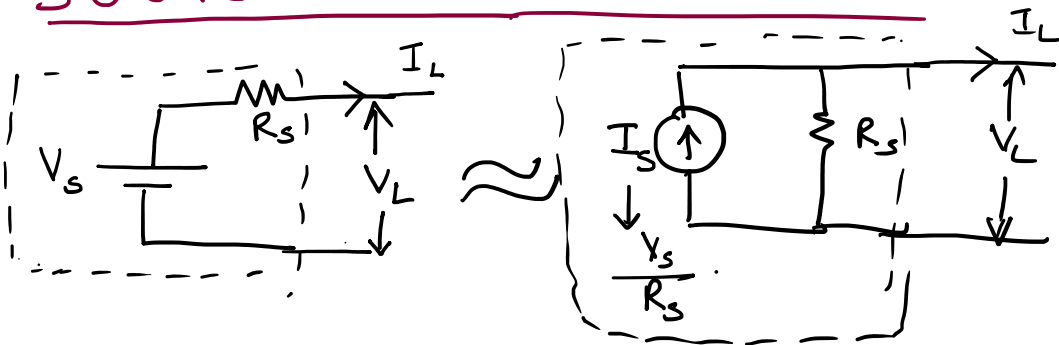

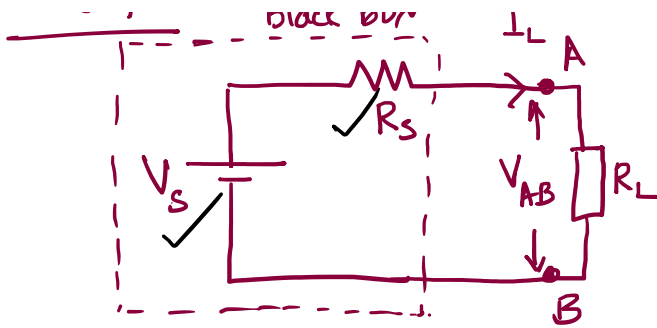


Circuit 1

$$I_L = \frac{V_s}{(R_s + R_L)} \quad \checkmark \text{---} \textcircled{1}$$

$$V_{AB} = I_L \cdot R_L = R_L \left[ \frac{V_s}{(R_s + R_L)} \right]$$

$$V_{AB} = \frac{V_s \cdot R_L}{(R_s + R_L)} \quad \checkmark \text{---} \textcircled{2}$$

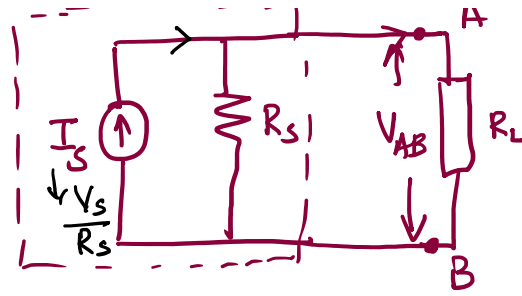

Circuit 2

$$I_L = I_s \cdot \frac{R_s}{(R_s + R_L)} \quad \text{---} \textcircled{1}'$$

$$V_{AB} = R_L I_L = \frac{R_L \cdot I_s R_s}{(R_s + R_L)}$$

$$V_{AB} = \frac{(I_s R_s) R_L}{(R_s + R_L)} \rightarrow \textcircled{2}'$$


$$\frac{CK+1}{I_L^{CK1}} \approx \frac{CK+2}{I_L^{CK2}} \quad \& \quad V_{AB}^{CK1} = V_{AB}^{CK2}$$

$$\frac{V_s}{(R_s + R_L)} = \frac{I_s R_s}{(R_s + R_L)}$$


$$\frac{\check{V}_s R_L}{(R_s + R_L)} = \frac{(\check{I}_s R_s) R_L}{(R_s + R_L)}$$

$$V_s = I_s R_s$$

$$V_s = I_s R_s$$

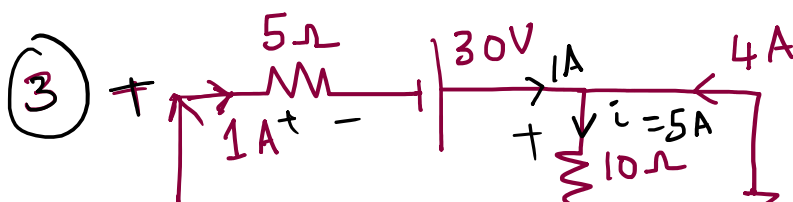

compute  $V_c$  &  $V_i$

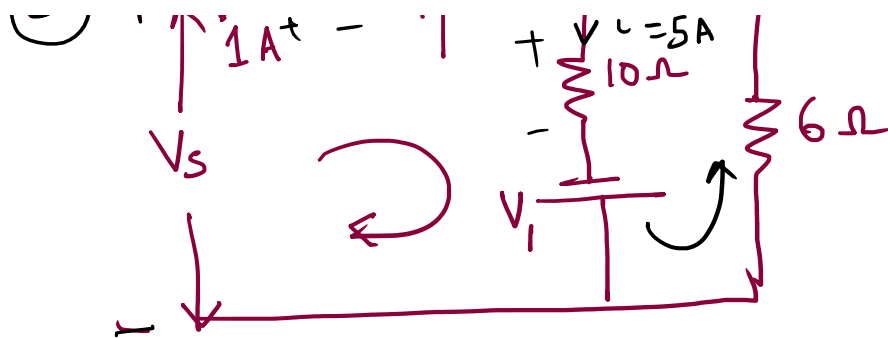

Compute  $V_S$  &  $V_1$

$$V_1 = 74V \checkmark$$


$$V_S = -49V \checkmark$$

$$V_S - 5 + 30 - 50 + V_1 = 0$$


$$V_S + V_1 = 25$$

$$V_1 - 24 - 50 = 0 \Rightarrow V_1 = 74V$$
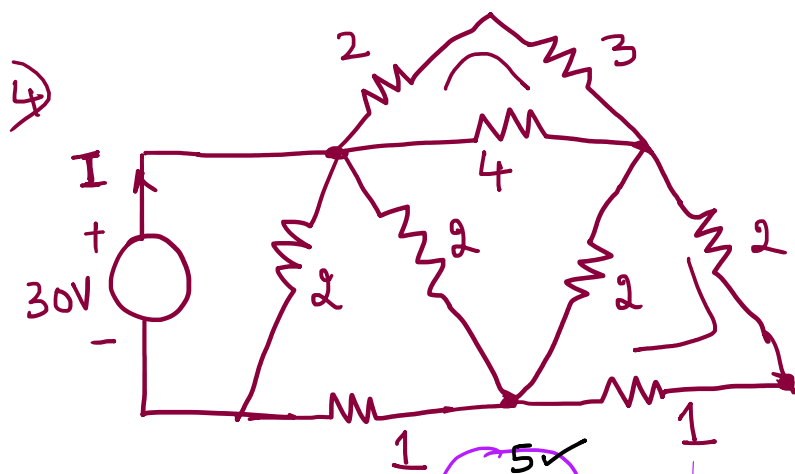
$$V_1 + V_S = 25 \Rightarrow V_S = -49V \checkmark$$



$I = ??$

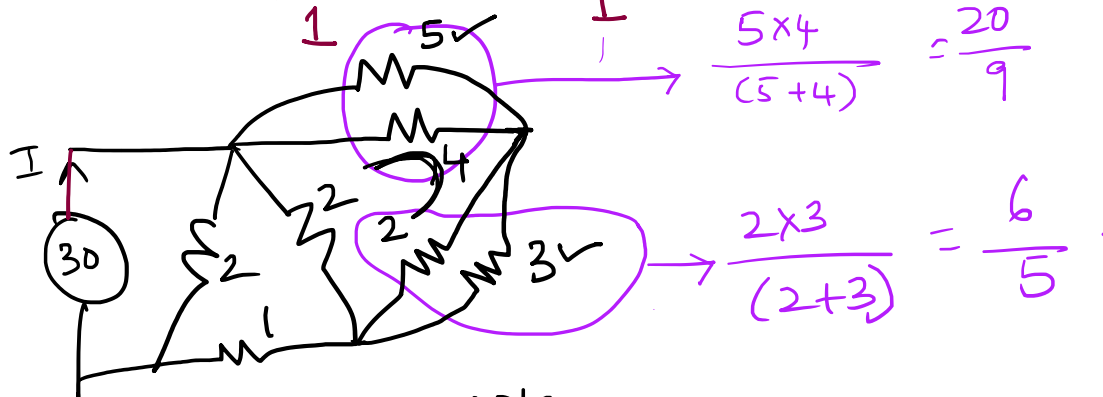


$$I = \frac{30V}{\frac{20}{9} + \frac{6}{5}} = \frac{100 + 54}{45} = \frac{154}{45}$$



$$\Downarrow \quad = \frac{154}{45} = 3.422 \, \Omega$$


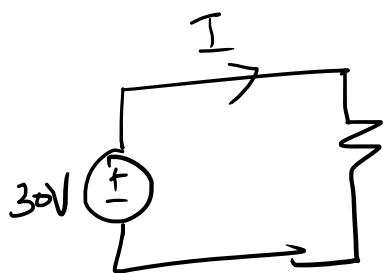
$$\Rightarrow R_{eq} = (2) \parallel (2 + 3.422) = 1.0614822 \, \Omega$$



$$1.06 \, \Omega ; I = \frac{30}{1.06} = \underline{\underline{28.26 \, A}}$$