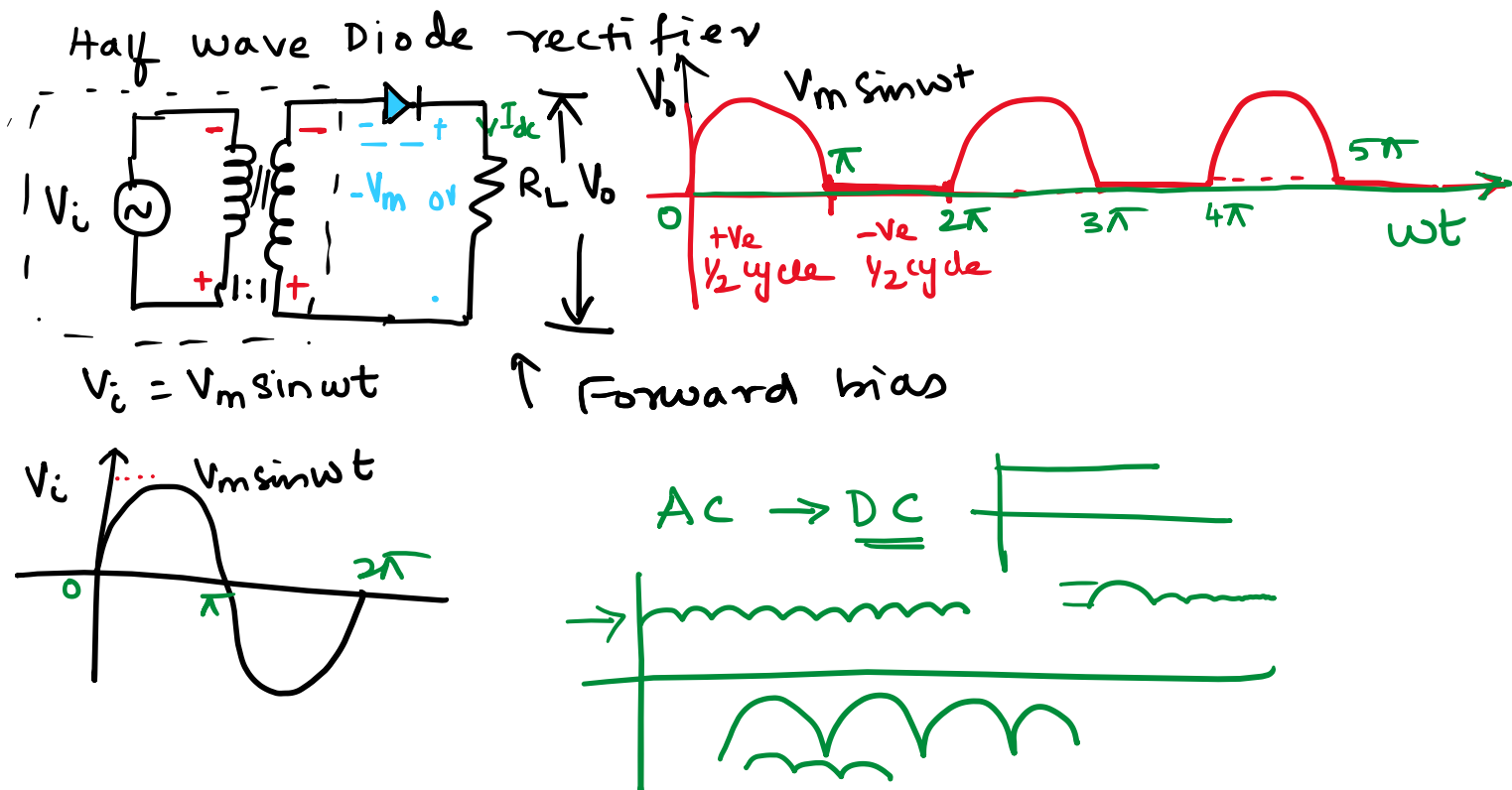


Chapter3: Semiconductor Devices and Circuits

1. Half-wave diode rectifier

- a. DC Output current
- b. DC Output voltage
- c. RMS current and Voltage
- d. Rectifier Efficiency
- e. Ripple factor
- f. Peak Inverse Voltage



- ✓ a. DC Output current / Avg .
- ✓ b. DC Output voltage / Avg .
- ✓ c. RMS current and Voltage
- ✓ d. Rectifier Efficiency
- e. Ripple factor
- f. Peak Inverse Voltage

$$V_i = V_m \sin \omega t$$


$$i_i = I_m \sin \omega t$$
$$= 0$$

$$0 \leq \omega t \leq \pi$$

$$\pi \leq \omega t \leq 2\pi$$

$$I_m = \frac{V_m}{(R_f + R_L)} ; R_f: \text{forward bias Diode resistance}$$

a) DC output current: / Avg. o/p current

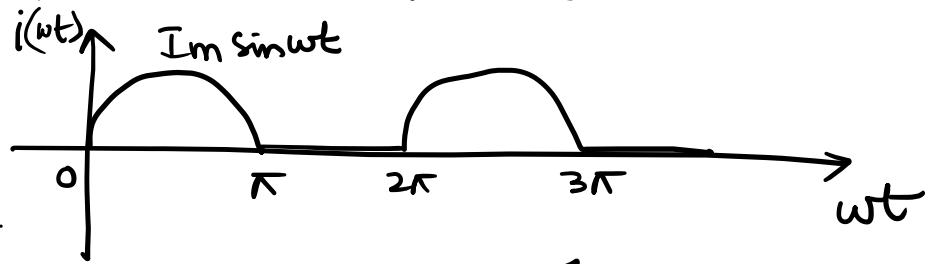

$$I_{dc} = \frac{1}{2\pi} \left[\int_0^{2\pi} i(\omega t) d\omega t \right]$$

$$= \frac{1}{2\pi} \left[\int_0^{\pi} I_m \sin \omega t d\omega t + \int_{\pi}^{2\pi} 0 d\omega t \right]$$


$$\checkmark I_{dc} = \frac{I_m}{2\pi} \left[-\cos \omega t \right]_0^{\pi} = \frac{I_m}{\pi} \checkmark$$

$$\checkmark I_{dc} = \frac{V_m}{(R_f + R_L) \pi} \quad \because R_f \ll R_L$$

$$= \frac{V_m}{\pi R_L}$$

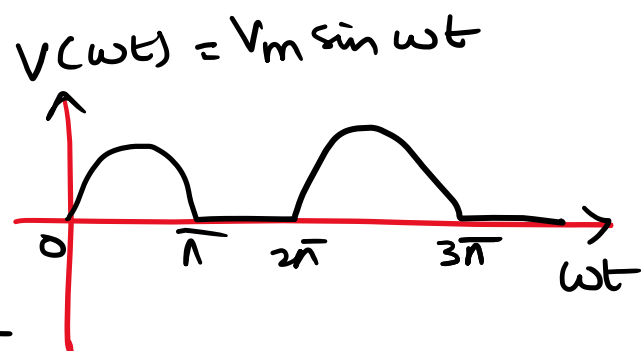(b) DC output Voltage:-

$$V_{dc} = I_{dc} \cdot R_L = \frac{V_m}{\pi R_L} \cdot R_L = \frac{V_m}{\pi}$$



(c) RMS current and Voltage

$$\begin{aligned}
 I_{rms} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (i_{cwt})^2 dwt} \\
 &= \left[\frac{1}{2\pi} \int_0^{\pi} (I_m^2 \sin^2 wt) dwt + \int_{\pi}^{2\pi} 0 dwt \right]^{1/2} \\
 &\quad \downarrow \\
 &\quad \left(\frac{1 - \cos 2wt}{2} \right) \\
 &= \left[\frac{I_m^2}{2\pi} \left[\frac{wt}{2} - \frac{\sin 2wt}{4} \right]_0^{\pi} \right]^{1/2} = \frac{I_m}{2} \\
 &\quad \boxed{I_{rms} = \frac{I_m}{2}}
 \end{aligned}$$


$$\rightarrow V_{rms} = I_{rms} \cdot R_L = \frac{I_m R_L}{2} = \frac{V_m}{2}$$

(iv) Rectifier efficiency $\eta = \frac{o/p}{i/p} =$

$$\eta = \frac{DC \ o/p}{AC \ i/p} = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} \cdot I_{dc}}{V_{rms} I_{rms}}$$


$$\eta = \frac{\frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}}{\frac{V_m}{2} \cdot \frac{I_m}{2}} \Rightarrow \eta = \frac{4}{\pi^2} = \underline{\underline{40.6\%}}$$

(v) Ripple

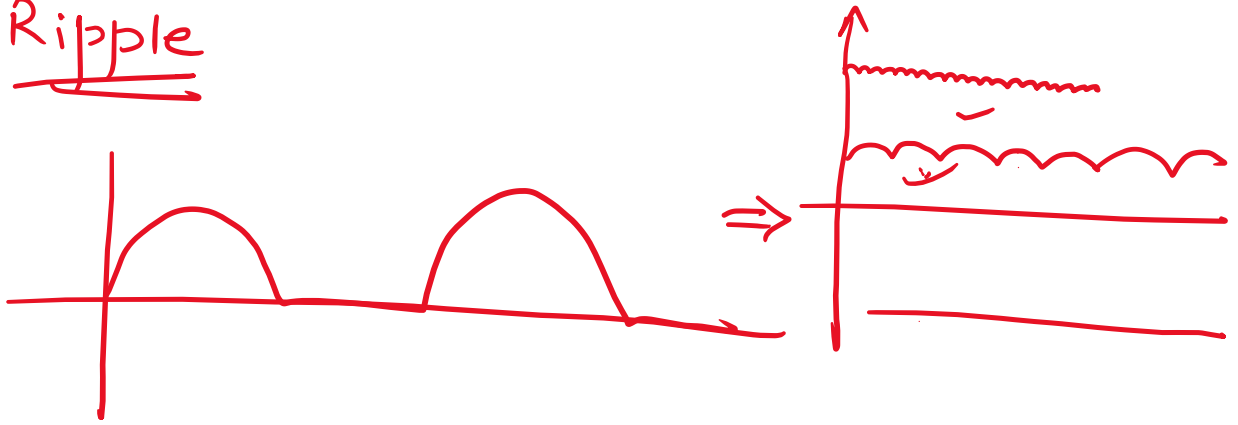

Gives idea about the waviness of the rectified Voltage & is defined as

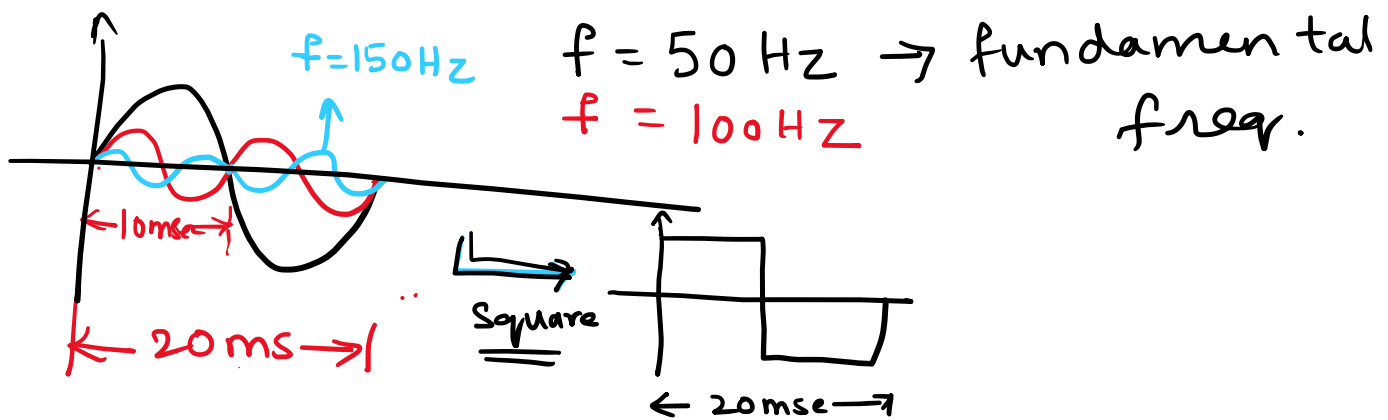
$$\gamma = \frac{I_{h,rms}}{I_{dc}} = \frac{V_{h,rms}}{V_{dc}}$$



$$f = \frac{1}{T} = \frac{1}{10 \text{ msec}} = 100 \text{ Hz}$$

$$f = 150 \text{ Hz}$$
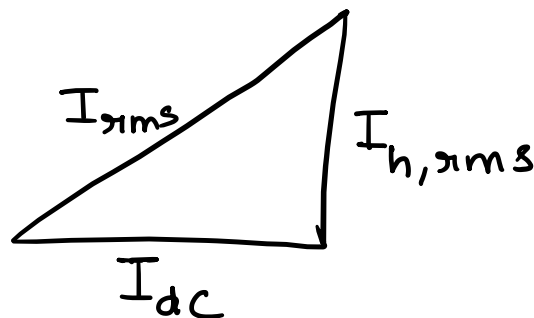
$$I_{rms} = \sqrt{I_{h,rms}^2 + I_{dc}^2}$$




$$\gamma = \frac{I_{h,rms}}{I_{dc}} = \frac{\sqrt{I_{rms}^2 - I_{dc}^2}}{I_{dc}}$$

$$\gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$





$$= \sqrt{\left(\frac{I_m/2}{I_m/\pi}\right)^2 - 1}$$

$$\boxed{\gamma = 1.21} \quad \checkmark$$

Peak Inverse Voltage :-


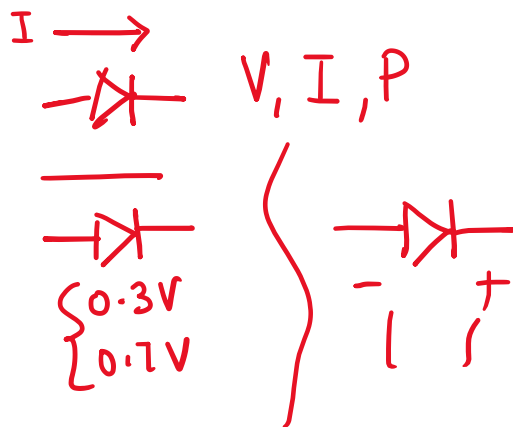


Reverse Bias

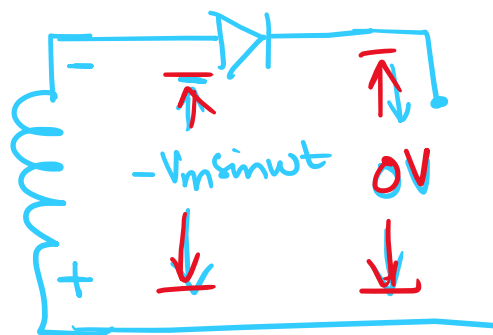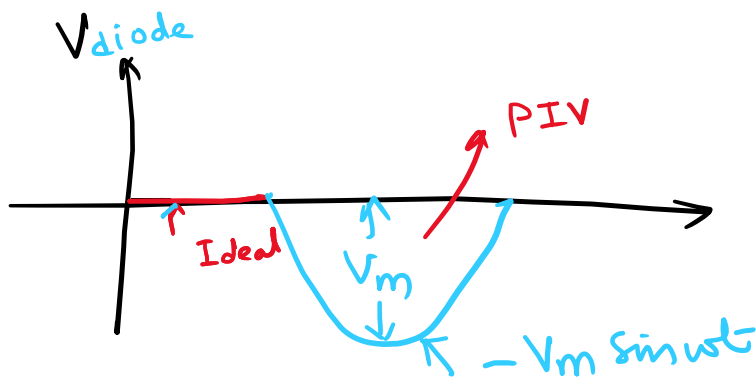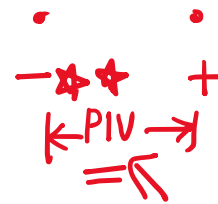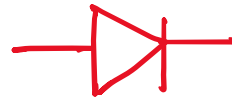

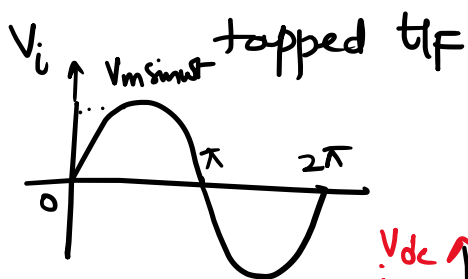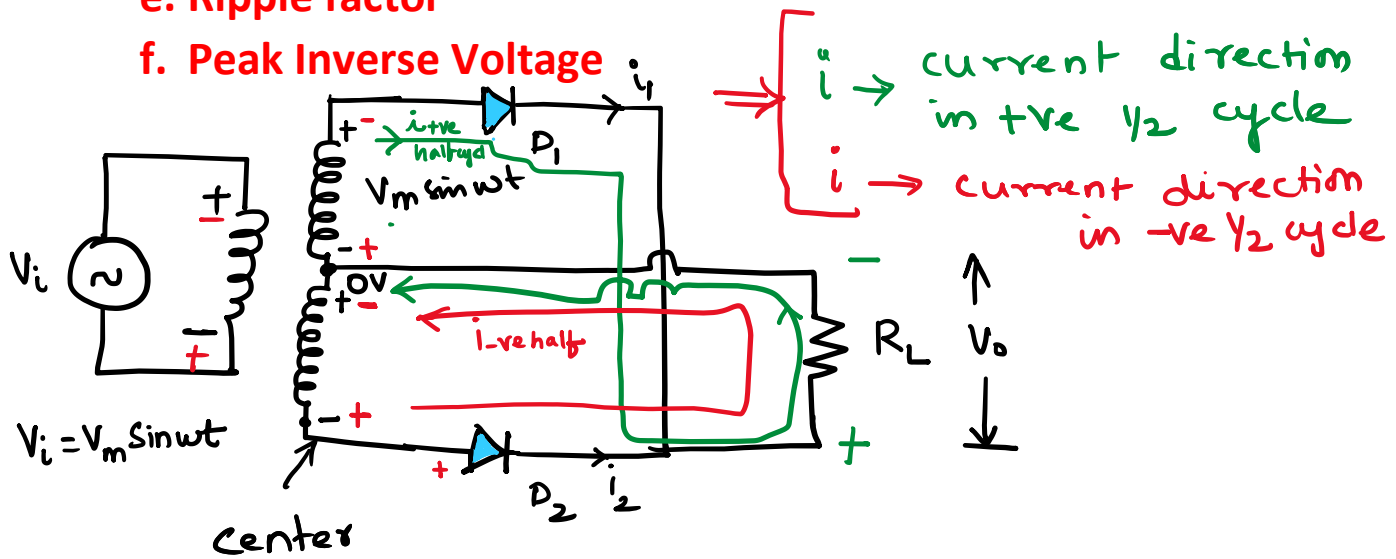
2. Full Wave diode rectifier

- DC Output current
- DC Output voltage
- RMS current and Voltage
- Rectifier Efficiency
- Ripple factor
- Peak Inverse Voltage



+ve. $\frac{1}{2}$ cycle of AC g/p

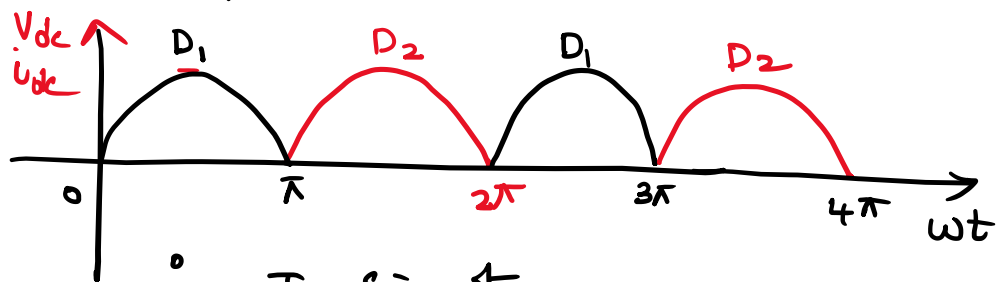$D_1 \rightarrow F.B$ & $D_2 \rightarrow R.B$



$$i = I_m \sin \omega t$$

$$V = V_m \sin \omega t$$

(a) DC or Average Current I_{dc} .

$$\begin{aligned}
 I_{dc} &= \frac{1}{2\pi} \int_0^{2\pi} (I_m \sin \omega t \, d\omega t) \quad \text{or} \quad \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t \, d\omega t \\
 &= \frac{I_m}{2\pi} \left[\left[-\cos \omega t \right]_0^{\pi} + \left[-\cos \omega t \right]_{\pi}^{2\pi} \right] = \frac{2I_m}{\pi} \checkmark
 \end{aligned}$$

(b) Average / Dc output Voltage.

$$V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega t \, d\omega t = \frac{2 V_m}{\pi} \checkmark$$

(c) RMS current & Voltage:

$$I_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} (I_m^2 \sin^2 \omega t) \, d\omega t} = \frac{I_m}{\sqrt{2}} \checkmark$$

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} (V_m^2 \sin^2 \omega t) \, d\omega t} = \frac{V_m}{\sqrt{2}} \checkmark$$

$$V_{rms} = \frac{I_m \cdot R_L}{\sqrt{2}} \checkmark$$


(v) Rectifier η = $\frac{P_{dc}}{P_{ac}} = \frac{V_{dc} \cdot I_{dc}}{V_{rms} I_{rms}}$

$$\eta = \frac{\frac{2 V_m}{\pi} \cdot \frac{2 I_m}{\pi}}{\frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}} = \frac{8}{\pi^2} = 81.14\%$$


(vi) Ripple factor: $\gamma = \frac{I_{h,rms}}{I_{dc}} = \frac{V_{h,rms}}{V_{dc}}$

$$\gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{\left(\frac{I_m/\sqrt{2}}{2I_m/\pi}\right)^2 - 1} = 48.38\%$$

(vii) Peak Inverse Voltage

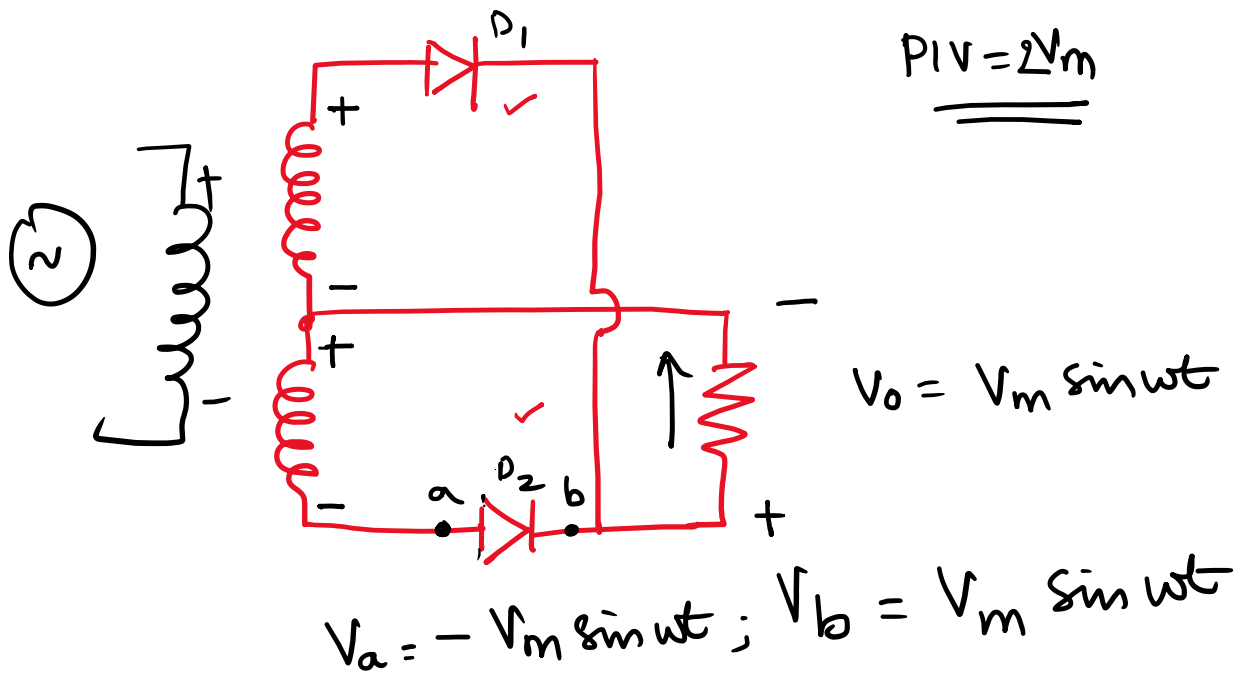
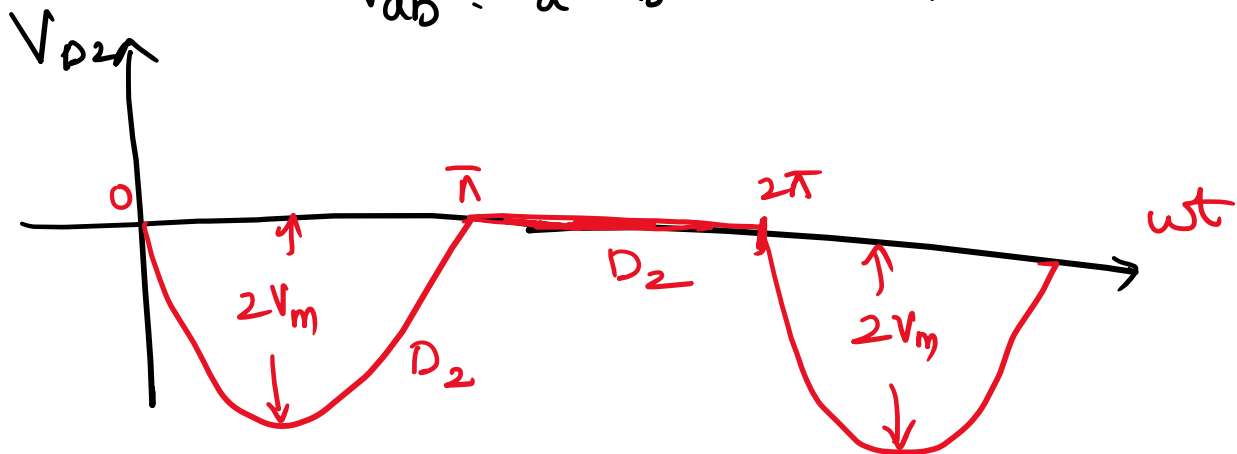
$$V_{ab} = V_a - V_b = -2V_m \sin \omega t$$



$$\left. \begin{array}{l} PIV \text{ in full wave} \\ \text{diode rectifier} \end{array} \right\} = 2V_m$$