



**राष्ट्रीय प्रौद्योगिकी संस्थान गोवा**  
**NATIONAL INSTITUTE OF TECHNOLOGY GOA**  
Farmagudi, Ponda, Goa – 403 401, India  
**Department of Electrical and Electronics Engineering**

**EE152**

**Basic Electrical Science Lab**

Website: <http://www.nitgoa.ac.in>

**Session – 4**

Phone : 0832-2404218

Fax : 0832-2404202

**DC Transient Analysis**

**1. A. Introduction:**

This session makes students to understand transient analysis of DC circuits through a Simulation platform, MATLAB/Simulink.

**1. B. Objectives:**

- Acquire a good knowledge on the transient behavior of the DC electrical circuits.
- Verification of the theoretical knowledge on transient behavior of DC electrical circuits in MATLAB/Simulink Platform.

**1. C. Theory:** Refer to the notes or necessary materials mentioned in EE151 course.

**1. D. Statement of Experiments:**

This session consists of two parts. [ $V_{in} = 10\text{ V}$ ,  $R = 10\ \Omega$ ,  $C = 10\ \mu\text{F}$ ,  $L = 10\text{ mH}$ ]

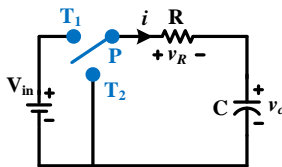


Fig. 4.a

- Using the circuit diagram shown in Fig. 4.a, characterize the circuit in Matlab/Simulink platform.
- Replace the capacitor by an inductor in Fig. 4.a, characterize the circuit in Matlab/Simulink platform.

**1. E. Procedure:**

**a. Part 1.D.a : DC RC circuit**

- Convert the circuit in Fig. 4.a into experimental circuit.
- Construct the experimental circuits in MATLAB/Simulink domain, and simulate it in following condition:
  - Connect P to  $T_1$  at  $t = 0$  sec, and run the simulation for 2 second.
  - Connect P to  $T_1$  at  $t = 0$  sec, and then connect P to  $T_2$  at  $t = 1$  sec. Run the entire simulation for 2 sec.
- Based on the simulation, fill up the Table - 4.1.
- Find expression of various responses in the circuit, like current voltage across elements.

**b. Part 1.D.b: DC RL circuit**

Follow the same procedure as mentioned in part 1.E.a., and based on the simulation, prepare an appropriate table and fill up it. Also, find expression of various responses.

**Assignments:**

Using circuit shown in Fig. 4.b, Connect P to  $T_1$  at  $t = 0$  sec, keep it for 0.2 sec and note down voltage across the capacitor and current through the inductor. Then connect P to  $T_2$  at  $t = 0.2$  sec and run the simulation for 2 second. Prepare an appropriate table and fill up it. Also, find expression of various responses under the condition when P is connected to  $T_2$ .

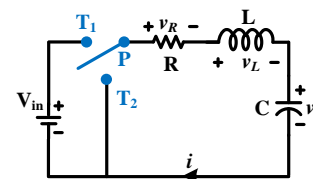


Fig. 4.b

Table - 4.1

Sl. No	Applied Voltage, $V_{in}$ (volts)	Time Constant, $\tau$ (Sec)		Rise Time, $T_r$ (Sec)		Settling Time, $T_s$ (Sec)	
		Theoretical	Simulation	Theoretical	Simulation	Theoretical	Simulation
1	10						
2	15						
3	20						