

## SEM 2 – 5 (RC 07-08)

### F.E. (Semester – II) (Revised in 2007-08) Examination, Nov./Dec. 2017 BASIC ELECTRONICS ENGINEERING


Duration : 3 Hours

Total Marks : 100

- Instructions :** 1) Answer 5 questions choosing atleast **one** from **each** Module.  
2) Assume data **if necessary**.

#### MODULE – I

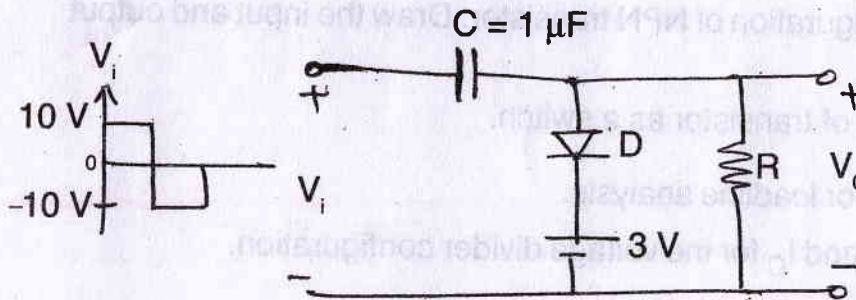
1. a) Determine the output waveform for the following circuit assuming RC time constant is very large and diode is ideal. 4



- b) Using Zener diode approximations find current through the diode of fig. when load resistance  $R_L$  is

- i)  $30\text{ k}\Omega$   
ii)  $5\text{ k}\Omega$ .

6

 

- c) What is a diode and how is the depletion region formed ? 4
- d) In a center tap full wave rectifier,  $R_L = 1\text{ k}\Omega$  and each diode has a forward biased dynamic resistance  $r_f = 10\text{ }\Omega$ . The voltage across each half of the secondary winding is  $220\sin\omega t$ . Determine  $I_m$ ,  $I_{dc}$ ,  $I_{rms}$  and Ripple factor. 6


P.T.O.



2. a) Explain the working of Half wave rectifier and derive the expression for Ripple factor and Efficiency. 10
- b) Why is a Filter required in a dc power supply ? Draw the circuit of a C filter and explain the output waveform. 5
- c) Draw and explain the operation of a Half wave voltage doubler. 5

## MODULE – II

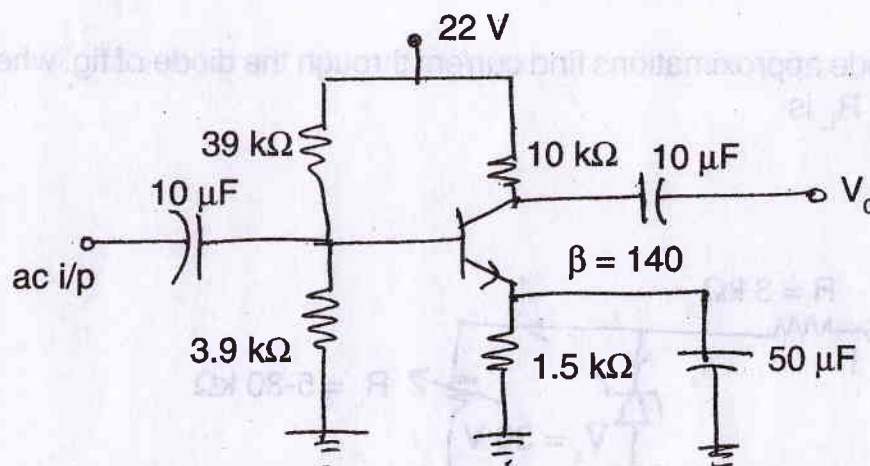3. a) What do you mean by stabilization of operating point ? Explain the reasons why stabilization of Q point is necessary. 4
- b) Explain Fixed Bias BJT biasing configuration. 6
- c) Explain CE configuration of NPN transistor. Draw the input and output characteristics. 6
- d) Explain working of transistor as a switch. 4
4. a) Explain Transistor loadline analysis. 5
- b) Determine  $V_{CE}$  and  $I_C$  for the voltage divider configuration. 5



- c) With the help of circuit diagram and waveforms explain how a transistor works as an amplifier. 5
- d) Explain basic transistor construction. 5

## MODULE – III

5. a) Draw and explain the drain to source characteristics of P-channel JFET. Also explain how transfer curve is obtained from the output characteristics. 7



b) For Fixed bias configuration given below, determine the following :

i)  $V_{GSQ}$

ii)  $I_{DQ}$


iii)  $V_{DS}$

iv)  $V_D$

v)  $V_G$

vi)  $V_S$

6

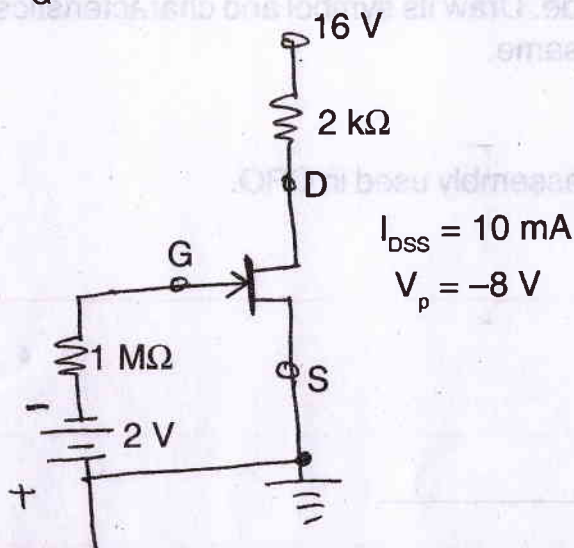

c) Explain the basic construction of n-channel JFET. Apply proper drain to source voltage and sketch the depletion region for  $V_{GS} = 0$  and  $V_{DS}$  at some positive voltages.

7

6. a) Explain construction of n-channel Enhancement type MOSFET. Also draw its drain characteristics.

8

b) Explain how CMOS can be used as an inverter.

5

c) For the n-channel depletion-type MOSFET shown below determine :

i)  $I_{DQ}$

ii)  $V_{GSQ}$

iii)  $V_{DS}$

7

