

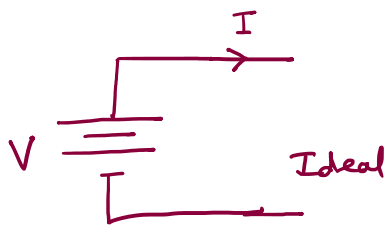


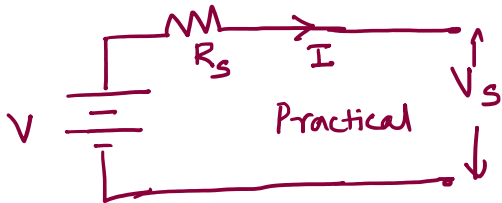Ideal Voltage Source & Ideal Current Source





Resistance of Source = 0




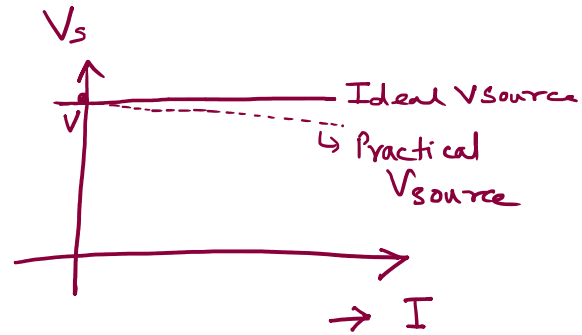


$$V_s = V - IR_s$$

Ideal current Source

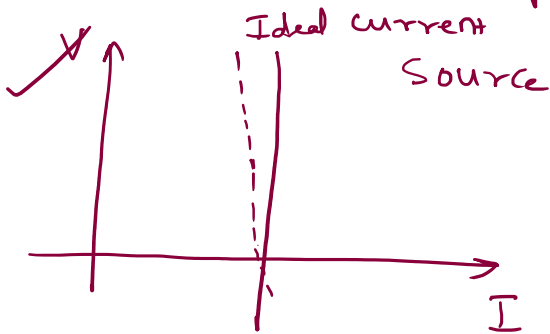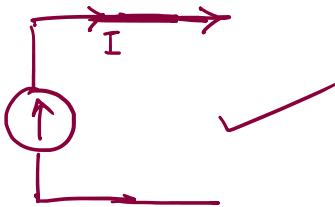

Practical Current Source

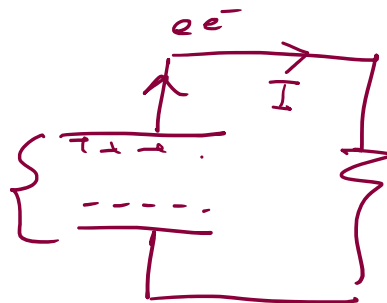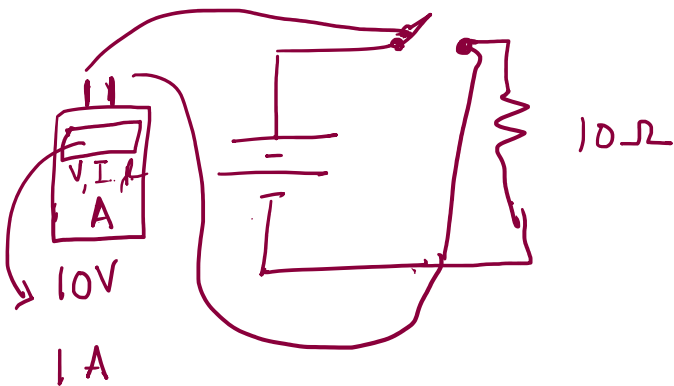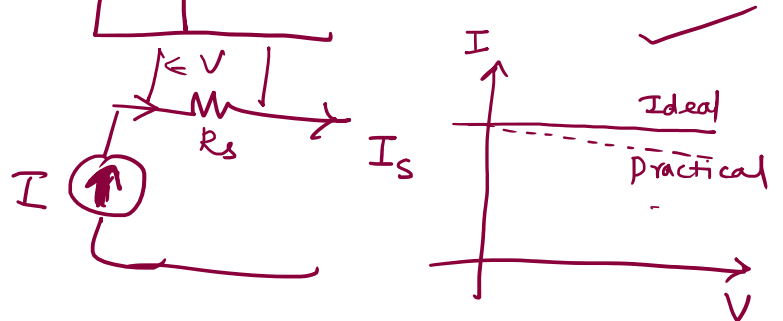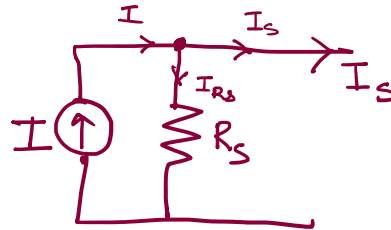

Can a Capacitor be considered as a Current Source ?

Power \Rightarrow Work done

1 Joule trans 1 coulomb over 1 Sec

$$\text{Power} \Rightarrow \frac{\text{Work done}}{\text{Time}}$$

1 Joule trans 1 colour over 1 sec


$$P = VI = \frac{V^2}{R} = I^2 R$$

$$P(t) = V(t) \cdot i(t)$$
$$= \frac{V^2(t)}{R} = i^2(t) \cdot R$$

Generate Power: Generator, DC / AC, battery, Solar Panel
 ↓ ↓ ↓
 turbine Diesel Gen, Dc Generator

Power Absorbing \Rightarrow Load, Motor, Lighting load, Resistance

Power is absorbed by the ckt

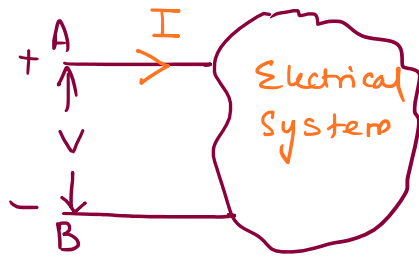


Power absorbed
by the electrical
system (ES) $\} = VI$

Power Generated by the ES $\} = -VI$

Power absorbed by ES $\rightarrow -10 \text{ W}$

$$P = -10 \text{ J/sec}$$

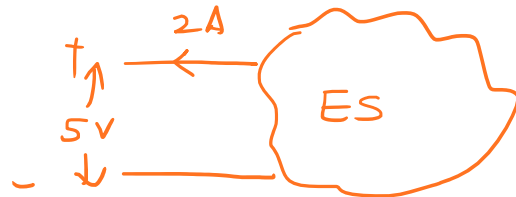

$$P = VI = (5)(-2)$$

$$I = -10 \text{ A/Sec}$$

$$V = 5 \text{ V}$$

$$P = V I$$



$$= (5)(-2)$$

Power Generated by ES = 10 W

$$\text{Power} = V I$$

$$= \frac{E}{Q} \cdot \frac{Q}{\text{Sec}} = \frac{\text{Joules}}{\text{Coulomb}} \times \frac{\text{Coulombs}}{\text{Sec}}$$

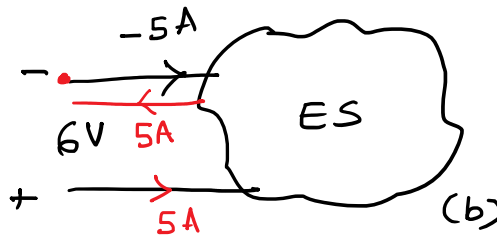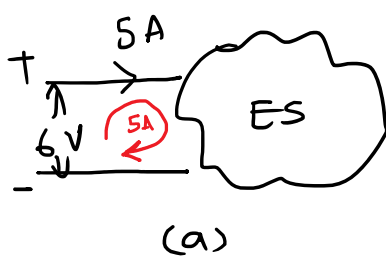
$$= \frac{\text{Joules}}{\text{Sec}} = \text{Watt}$$




Power absorbed by ES

$$30 \text{ W}$$

(a)

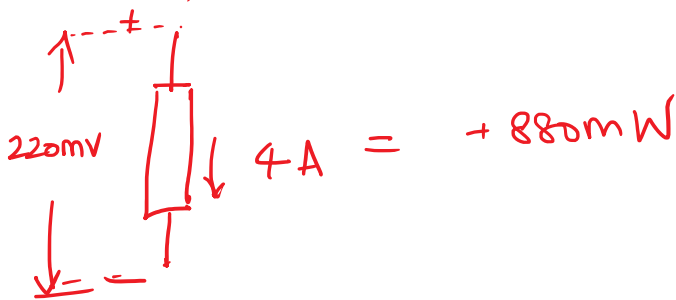

$$30 \text{ W}$$

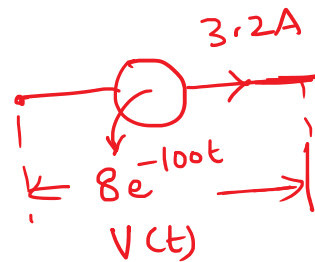

$$P(t) = V(t) i(t)$$

$$= 8 e^{-100t} \times 3.2 \text{ A}$$

$$= 25.6 e^{-100t}$$

What is the power at $t = 5 \text{ msec}$


$$P(t) = 25.6 e^{-(100 \times 5 \times 10^{-3})}$$

$$= 25.6 e^{-0.5}$$


$$= 25.6 \text{ e}$$

RESISTANCE


$$\text{OHM LAW: } \underline{V = IR}$$

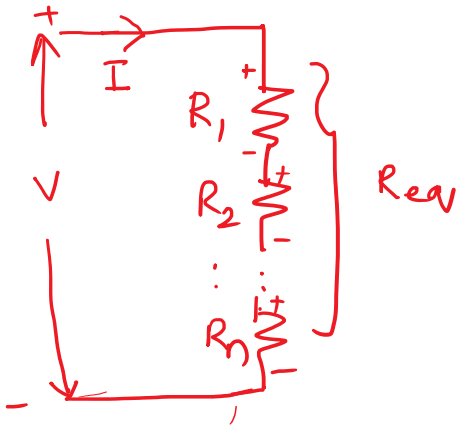

$$V = I R_{eq}$$

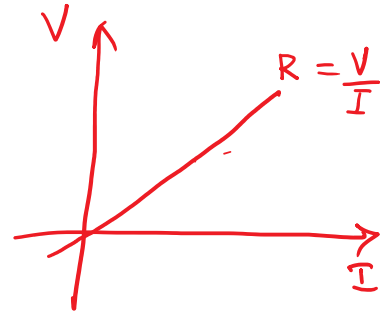

Kirchoff's current Law :-

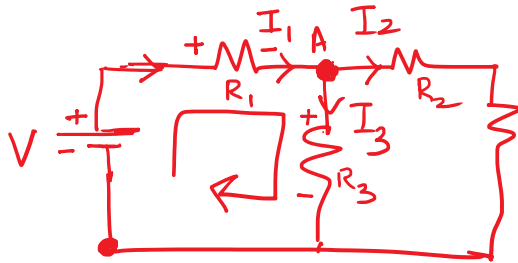

Direction of

Current entering A: +ve

dire. of current leaving 'A' } \Rightarrow -ve

Algebraic sum of currents entering a node = 0

$$I_1 - I_2 - I_3 = 0$$

Kirchoff's Voltage Law

$$V - I_1 R_1 - I_3 R_3 = 0$$

Equivalent Resistance of Series 'R' ckt



$$V = I R_{eq}$$

$$V = I R_{eq}$$

$$V = IR_1 + IR_2 + IR_3 + \dots + IR_n$$

$$I R_{eq} = I(R_1 + R_2 + \dots + R_n)$$

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

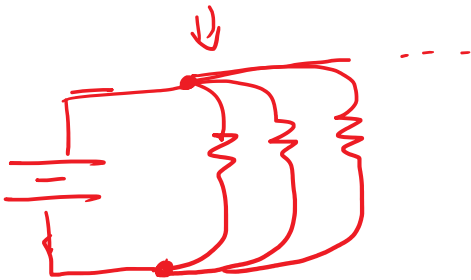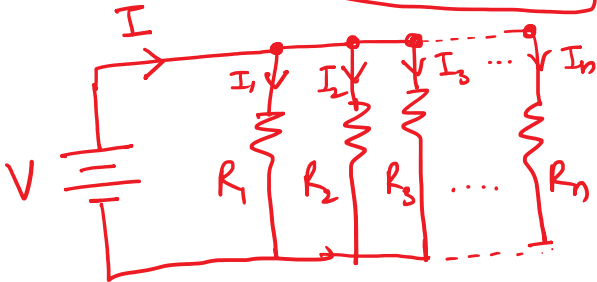

Equivalent Resistance in ||

KCL


$$I = I_1 + I_2 + \dots + I_n$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \dots + \frac{V}{R_n}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

R, L, C

Equivalent Inductance

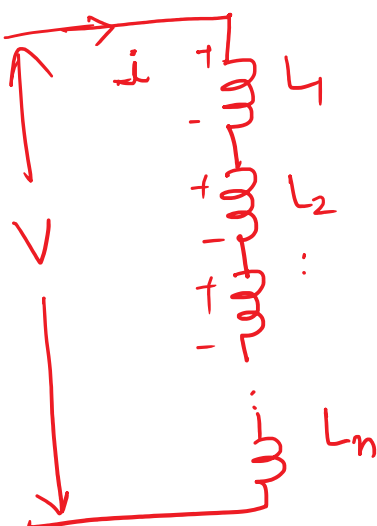

$$V = L_{eq} \frac{di}{dt}$$

$$V = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$

$$+ \dots + L_n \frac{di}{dt}$$


$$L_{eq} = L_1 + L_2 + \dots + L_n$$

$$i = C \frac{dv}{dt}$$

$$C = \frac{q}{V}$$



$$L_{eq} = L_1 + L_2 + \dots + L_n$$

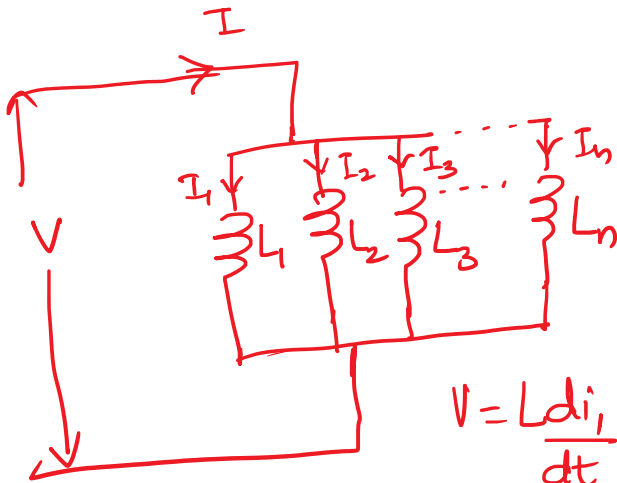


$$I = I_1 + I_2 + \dots + I_n$$

$$\frac{dI}{dt} = \frac{dI_1}{dt} + \frac{dI_2}{dt} + \dots + \frac{dI_n}{dt}$$

$$\frac{V}{L_{eq}} = \frac{V}{L_1} + \frac{V}{L_2} + \dots + \frac{V}{L_n}$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

CAPACITANCE

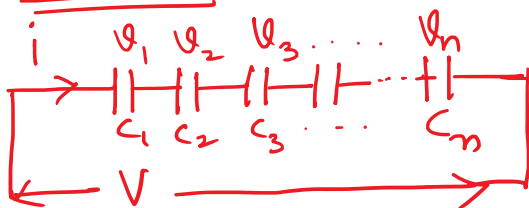

$$C = \frac{q}{V} \Rightarrow V = \frac{q}{C}$$

$$V = \frac{q}{C_{eq}}$$


Applying KVL

$$V = V_1 + V_2 + \dots + V_n$$

$$\frac{q}{C_{eq}} = \frac{q}{C_1} + \frac{q}{C_2} + \dots + \frac{q}{C_n}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$
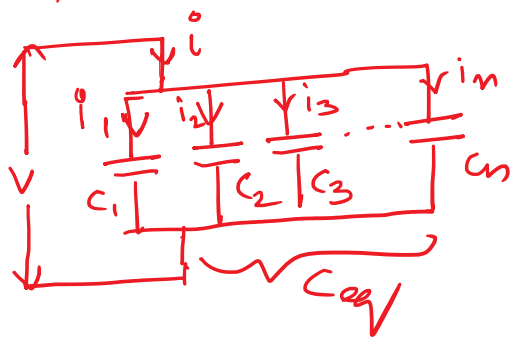
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$



$$q = q_1 + q_2 + \dots + q_n$$


$$V = \frac{q}{C}$$

$$q = q_1 + q_2 + \dots + q_n$$

$$V C_{eq} = V C_1 + V C_2 + V C_3 + \dots + V C_n$$

$$C_{eq} = C_1 + C_2 + \dots + C_n$$


Kirchoff's Voltage Law

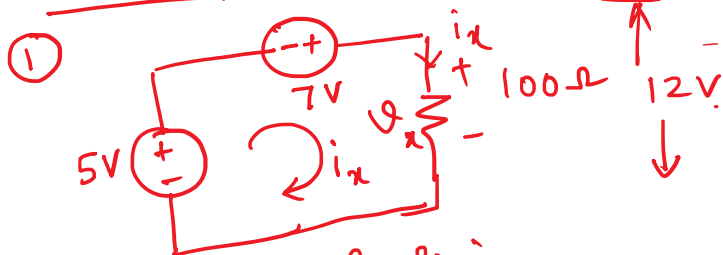

Compute v_x & i_x

$$5 + 7 - v_x = 0 \Rightarrow v_x = 12V$$

$$i_x = \frac{12}{100} = 0.12A$$

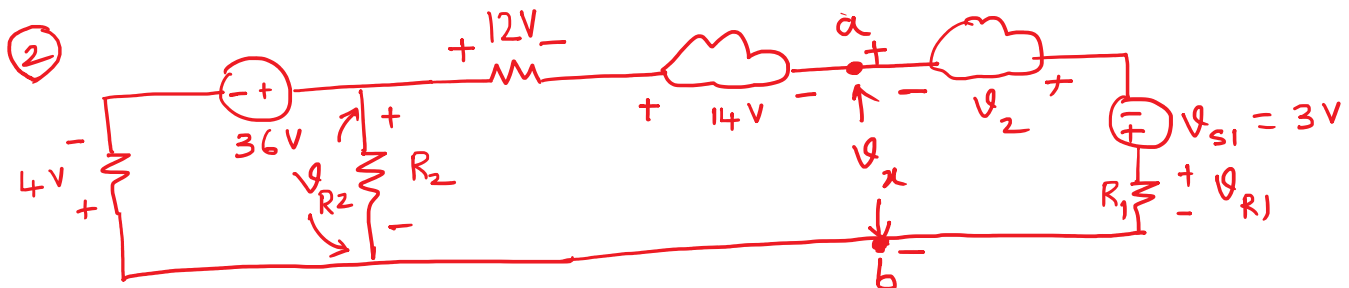

Find v_x & v_{R1}


a) In this circuit, find V_{R2} & V_x .

b) Find V_2 if $V_{R1} = 1V$

$$(a) \quad V_{R2}: -4V + 36V - V_{R2} = 0 \Rightarrow V_{R2} = 32V$$

$$V_x: 32 - 12 - 14 - V_x = 0 \Rightarrow V_x = 6V$$
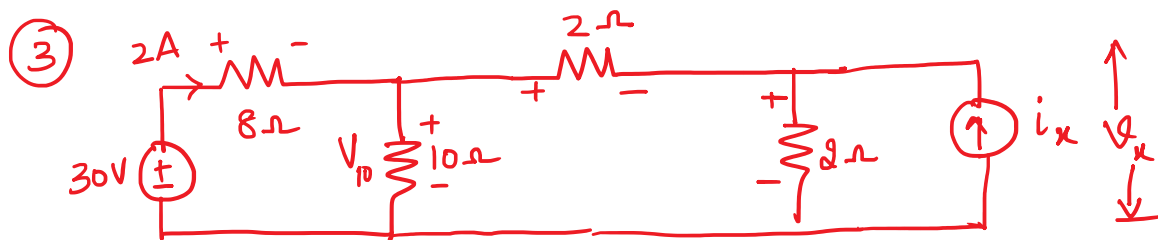
$$(b) \quad V_2: 6 + V_2 + 3 - 1 = 0 \Rightarrow V_2 = -8V$$



Determine V_x & i_x .