

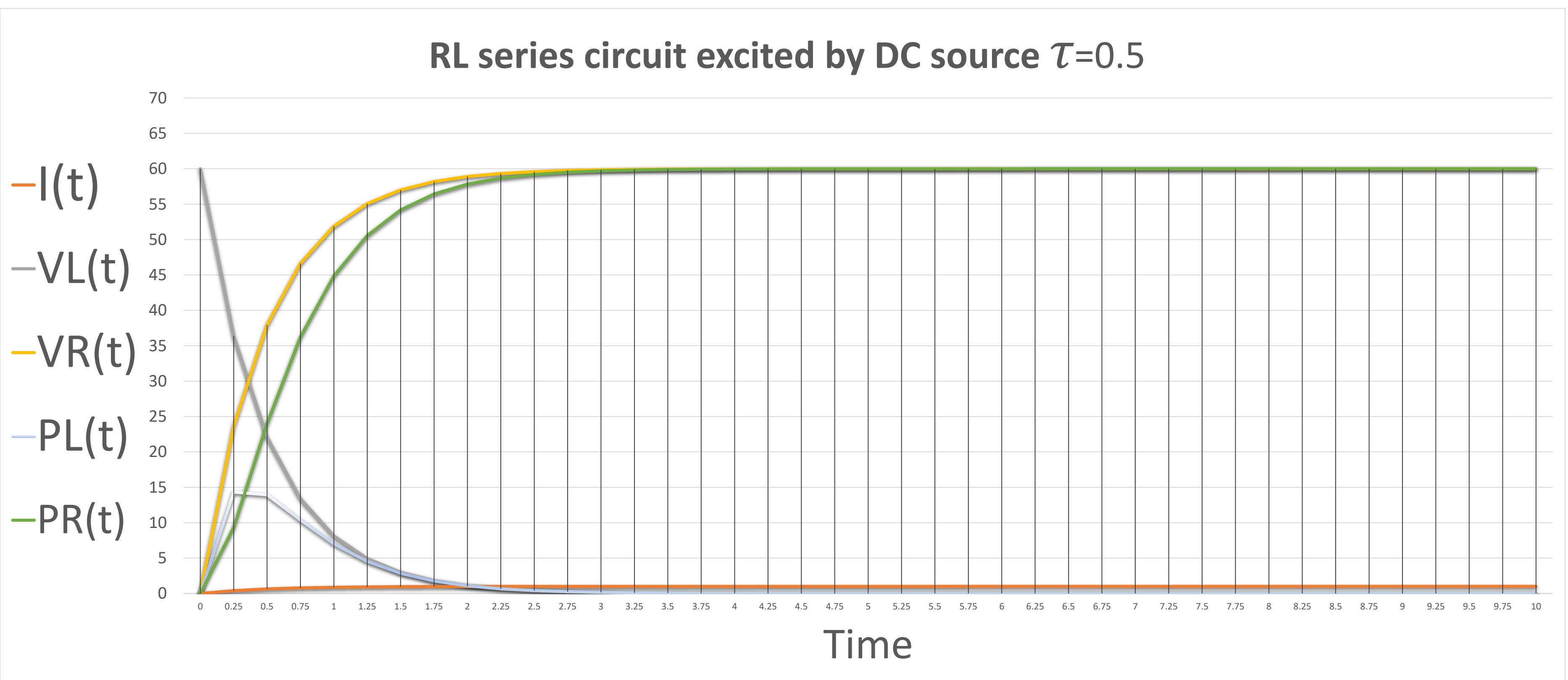


NAME : ZUBIN SHAH


ROLL : 20CSE1030

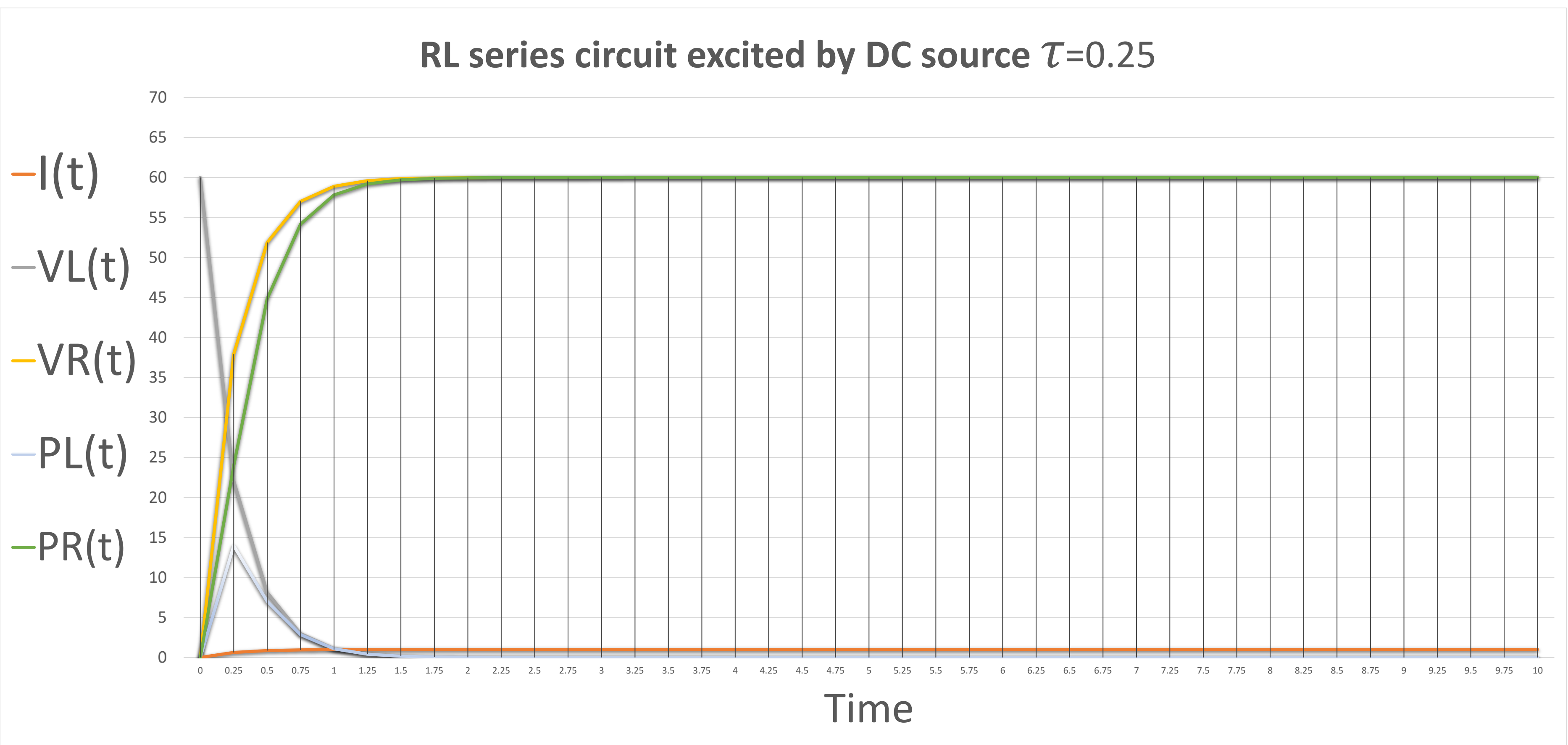

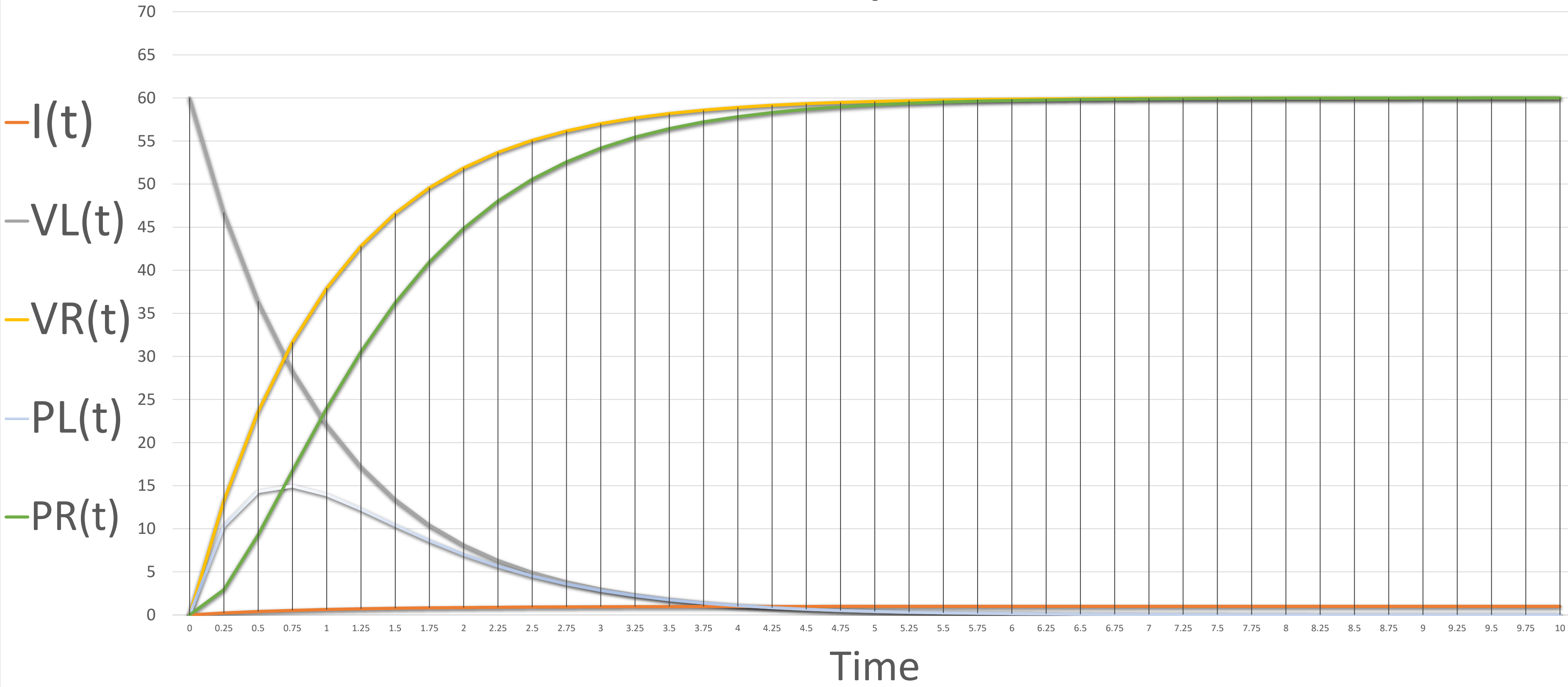
RL series circuit excited by DC source $\tau=1$



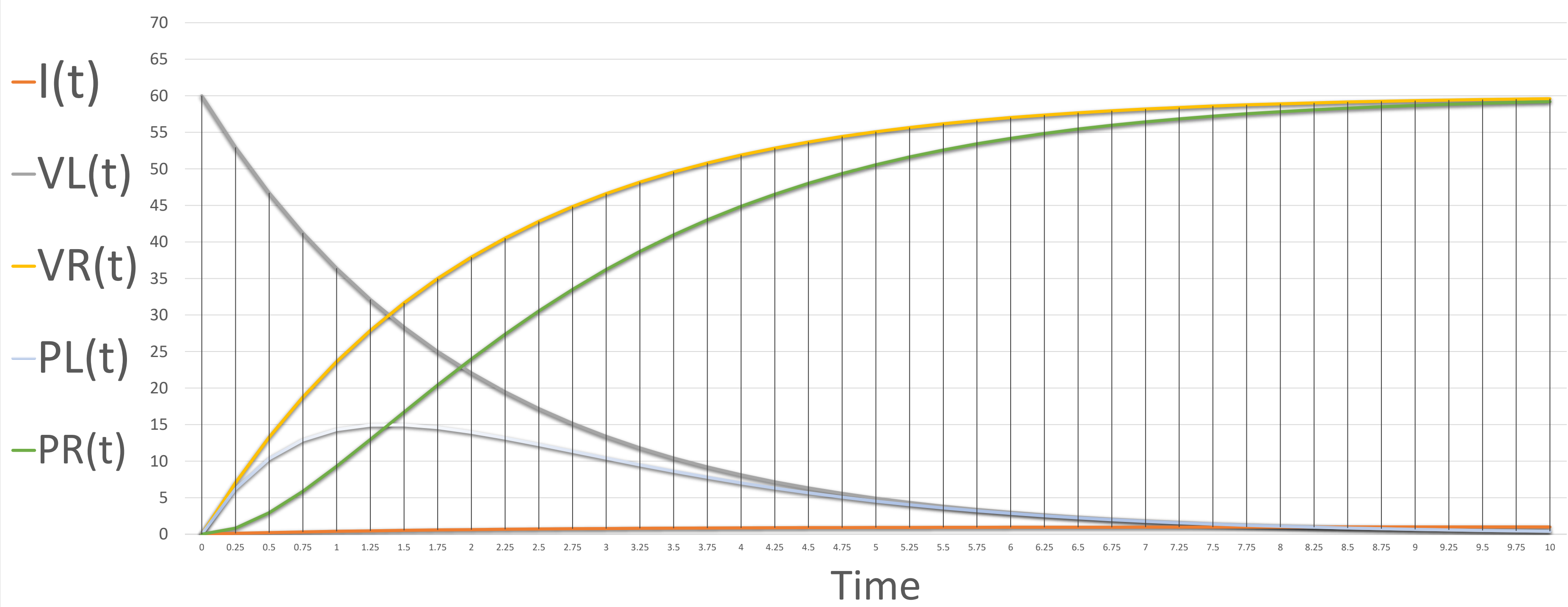
RL series circuit excited by DC source $\tau=2$



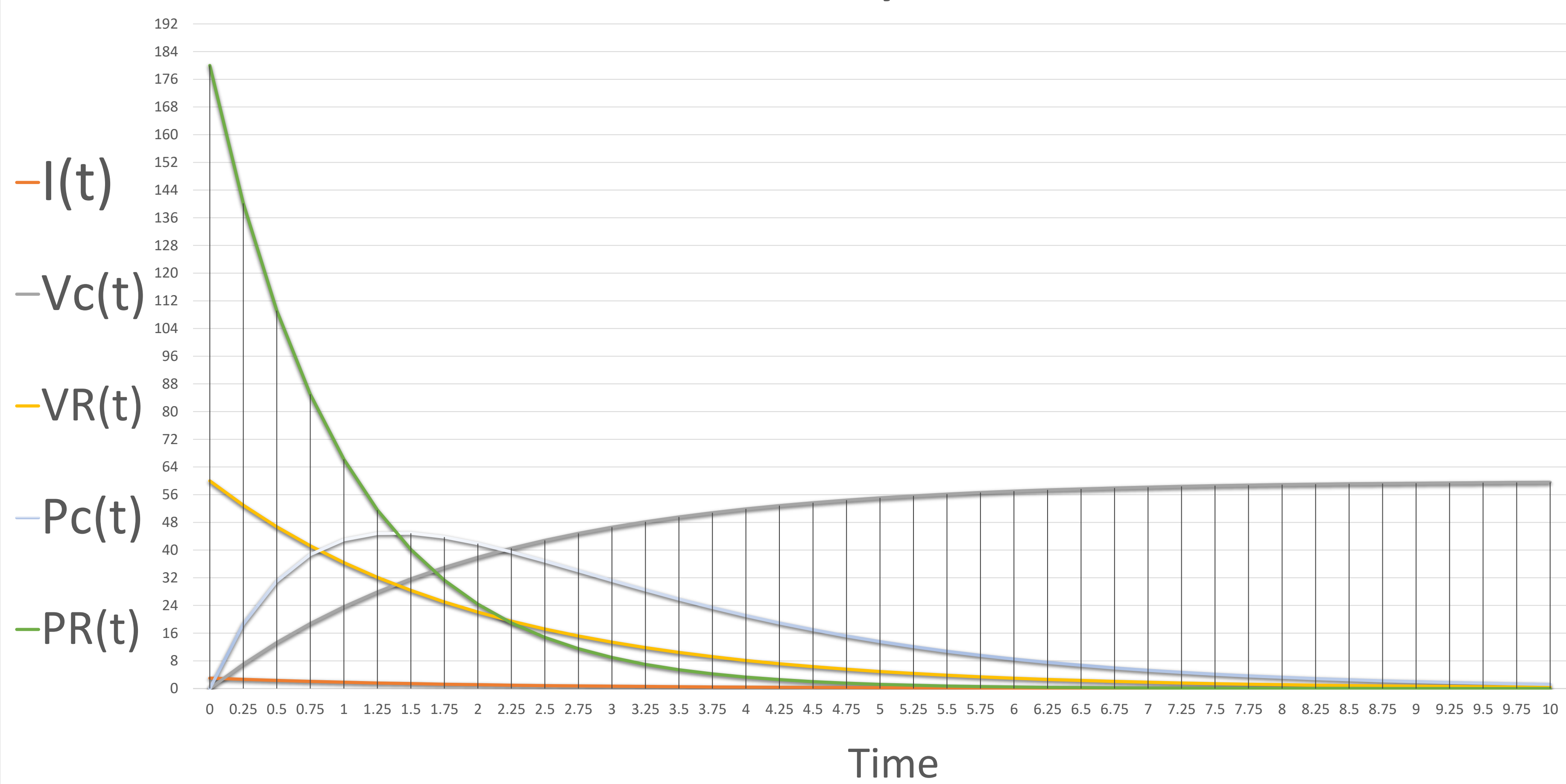
RC series circuit excited by DC source $\tau=2$



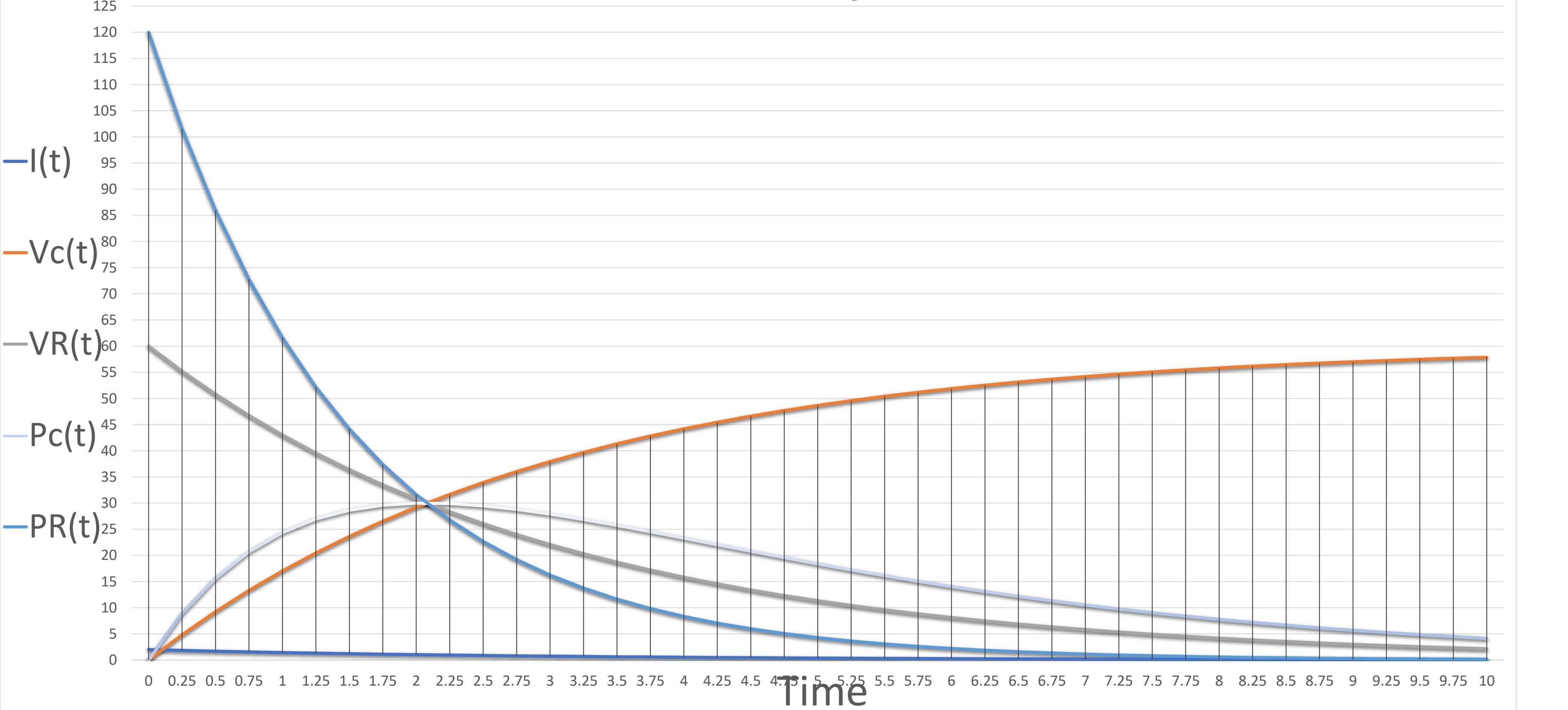RC series circuit excited by DC source $\tau=3$



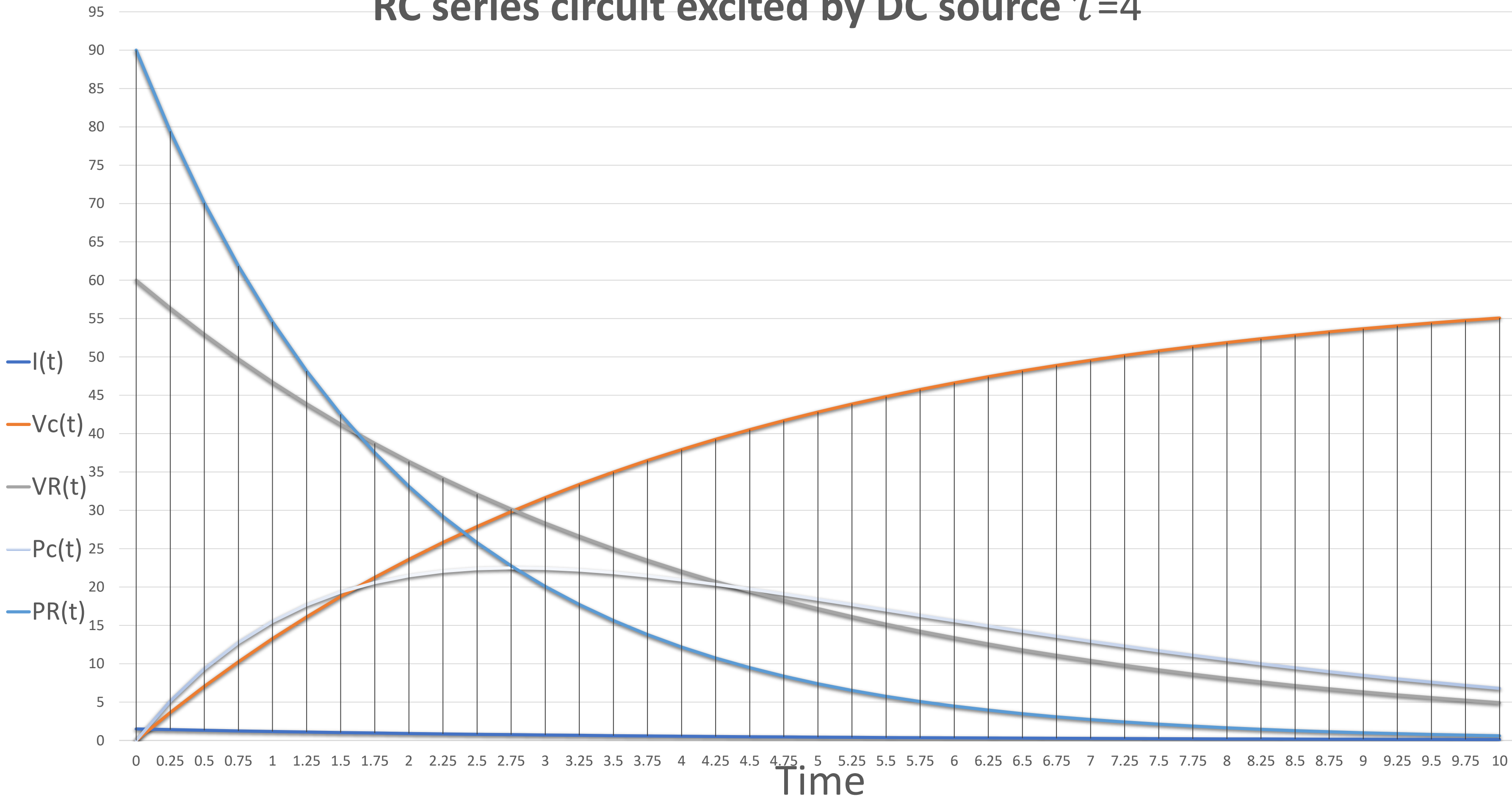RC series circuit excited by DC source $\tau=4$



RC series circuit excited by DC source $\tau=5$

