

# F.E. (Semester – II) (Revised in 2007-08) Examination, May/June 2017 BASIC ELECTRONICS ENGINEERING

Duration: 3 Hours


Max. Marks: 100

Instructions: 1) Answer 5 questions choosing atleast one from each Module.


2) Assume data if necessary.

#### MODULE-1

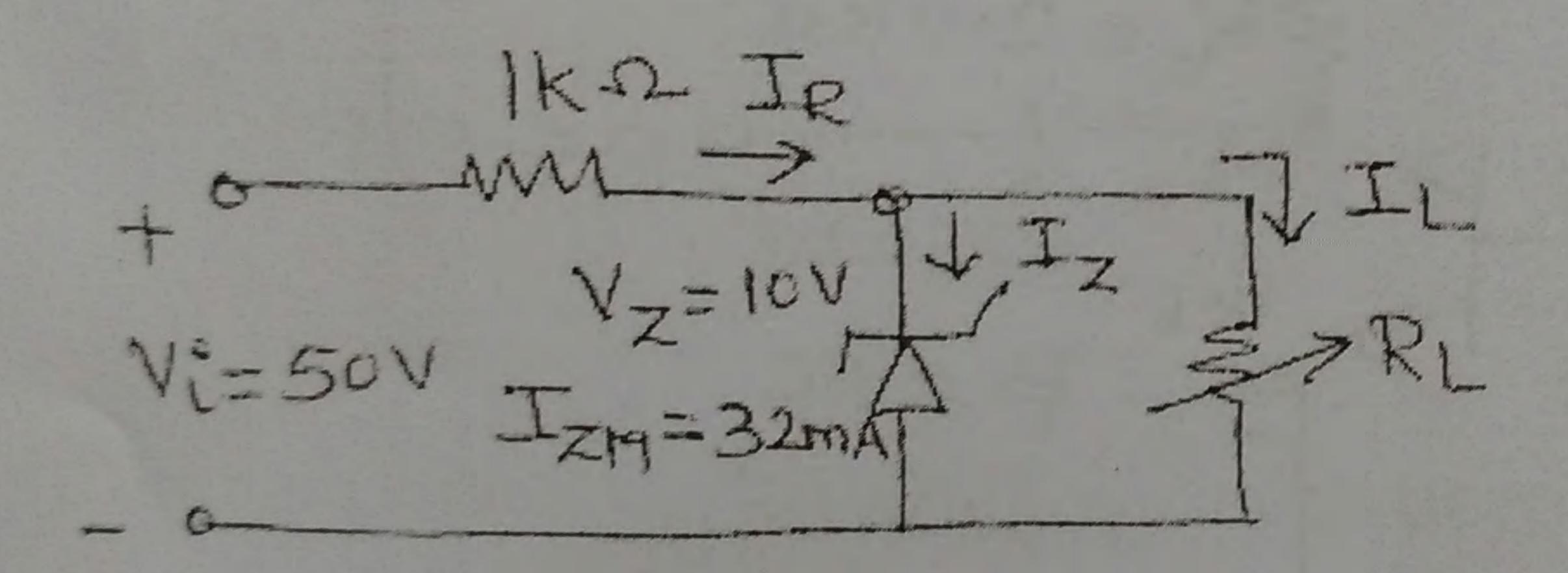- 1. a) Prove that the Ripple factor of a Full Wave Rectifier is 0.482.b) Explain the operation of a half wave Voltage doubler.
  - c) Explain with circuit diagram the details of drawing loadline and determine the point of operation on the diode characteristics.
  - d) Determine the range of R<sub>L</sub> and I<sub>L</sub> that will result in V<sub>RL</sub> being maintained at 10v. Determine the maximum wattage rating of the diode.



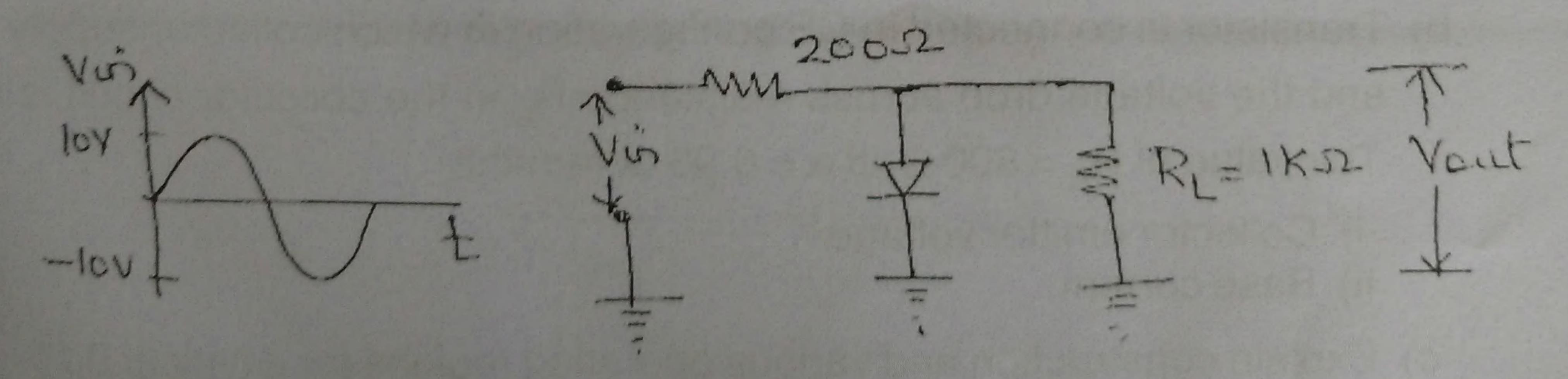a) The Positive Shunt Clipper shown in fig. below has the input waveform as indicated. Determine the values of V<sub>out</sub> for each of the input alternations.



b) Show that the maximum rectification efficiency of a half wave Rectifier is 40.6%.

- c) Differentiate between Zener breakdown and Avalanche breakdown.
- d) Draw V-I characteristics of PN Junction diode and explain piecewise linear equivalent circuit of a diode.

### MODULE-II

3. a) Explain CE configuration of a NPN transistor. Draw the input and output characteristics.

b) Explain how transistor can be used as an amplifier. 5

- c) With the help of necessary equations obtain the relation between  $\beta$  and  $\alpha$ . 4
- d) Determine the following for the fixed bias configuration of fig.

i)  $I_{BQ}$  and  $I_{CQ}$  ii)  $V_{CEQ}$  iii)  $V_{B}$  and  $V_{C}$  iv)  $V_{BC}$ 

$$R_{B}=24dm^{2}$$

$$R_{C}=2\cdot2k\Omega$$

$$C=10\mu$$

$$C=10\mu$$

$$R_{C}=10\mu$$

$$R_{C}=2\cdot2k\Omega$$

$$C=10\mu$$

$$C=10\mu$$

- 4. a) What do you mean by Stabilization of operating point? Explain the reasons why Stabilization of Q point is necessary?
  - b) Transistor is connected in CE configuration in which collector supply is 8V and the voltage drop across resistance  $R_{\rm C}$  in the collector circuit is 0.5V. The value of  $R_{\rm C}$  = 800  $\Omega$ . If  $\alpha$  = 0.96 determine
    - i) Collector emitter voltage
    - ii) Base current.

c) Explain construction and various operating regions for a typical BJT.

d) Compare the Biasing methods. Which is the best biasing technique? Explain any one biasing technique.

## 

### MODULE-III

5. a) With the help of neat diagram, explain the operation of P channel JFET. Also show internal depletion regions and explain their shapes.


8

b) With the help of neat diagram and set of equations explain self bias configuration of JFET.

7

- c) For fixed bias configuration given below, determine the following:
  - i) V<sub>GSC</sub>
- ii) IDO
- iii) V<sub>DS</sub>

L

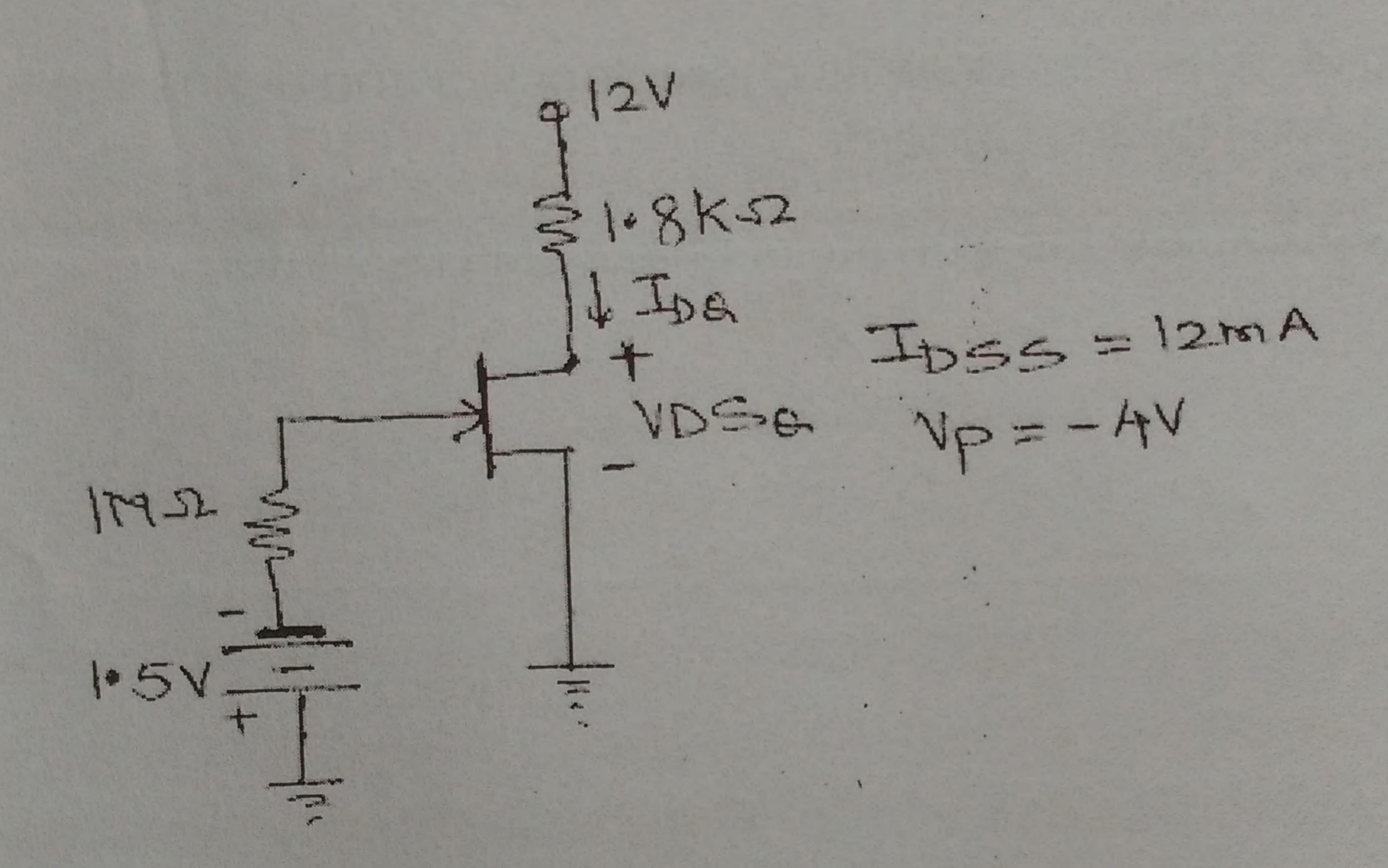

6. a) Explain with a sketch why I<sub>D</sub> exceeds beyond I<sub>DSS</sub> if positive voltage is applied at the gate of n-channel depletion type MOSFET.


6


b) With the help of neat sketches comment on the Polarity of various voltages and direction of current for n channel and P channel JFET.

6

c) Determine  $I_{DQ}$   $V_{GSQ}$  and  $V_{DS}$  for Enhancement type MOSFET given below :

8

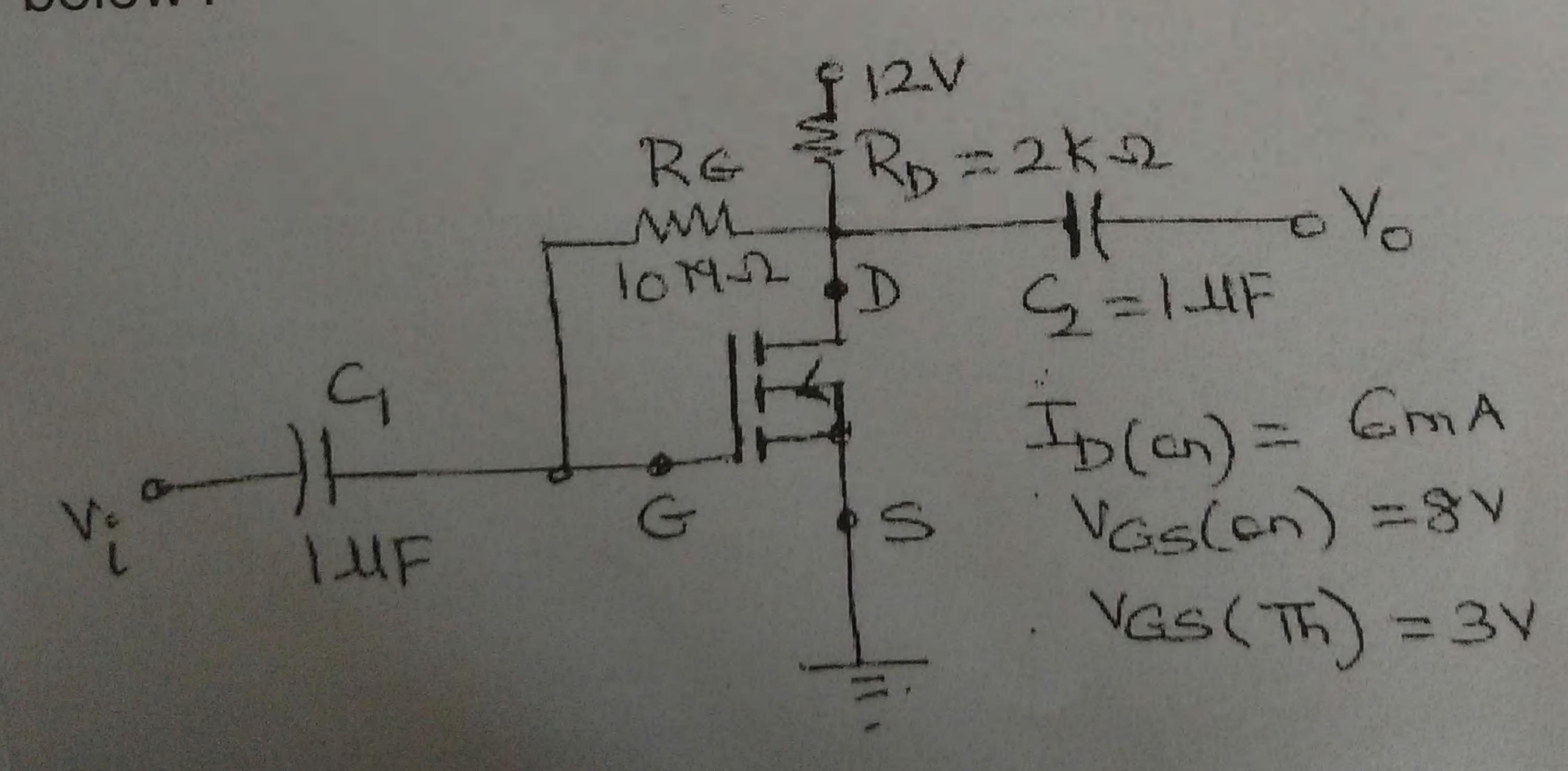

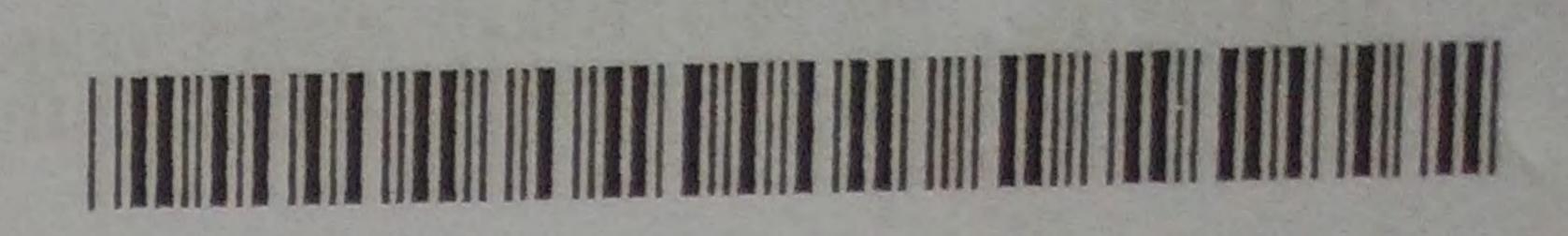

### MODULE-IV

	a)	Explain the block diagram of OPAMP.	
	b)	Give the manufacturing steps involved in Fabrication of discrete diode.	
	c)	With the help of neat diagram explain the working of transmissive type field effect LCD.	*
	a)	Explain how internal synchronization is achieved in CRO.	6
	b)	Explain working of SCR. Also draw its characteristics and define the term Latching current and Holding Current.	8
	C)	With neat diagram explain the working of phase shift oscillator.	6