



राष्ट्रीय प्रौद्योगिकी संस्थान गोवा
NATIONAL INSTITUTE OF TECHNOLOGY GOA
Farmagudi, Ponda, Goa – 403 401, India
Department of Electrical and Electronics Engineering

Website: <http://www.nitgoa.ac.in>

Phone : 0832-2404218

Fax : 0832-2404202

EE152

Basic Electrical Science Lab

Session – 2

Verification of Kirchhoff's Laws

1. A. Introduction:

This session makes students to understand Kirchhoff's Laws (KCL & KVL) and to verify through a simulation platform, MATLAB/Simulink.

1. B. Objectives:

- a. Acquire good knowledge on Kirchhoff's Laws
- b. Verification of the two laws in MATLAB/Simulink Platform

1. C. Theory: Refer to the notes or necessary materials mentioned in EE151 course.

1. D. Statement of Experiments:

This session consists of two parts. [$V = 100 \text{ V}$, $R_x = (10 \times x) \Omega$]

- a. Using the circuit diagram shown in Fig. 2.a, verify KVL in Matlab/Simulink platform.
- b. Using the circuit diagram shown in Fig. 2.b, verify KCL in Matlab/Simulink platform

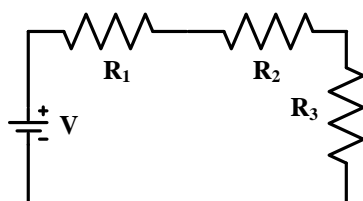


Fig. 2.a

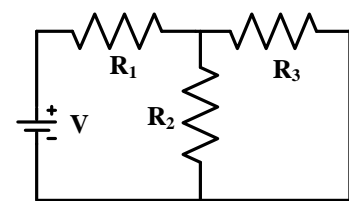


Fig. 2.b

1. E. Procedure: The general procedure for the two parts of this experiment is same.

- a. Convert the circuit shown in Fig. 2 into experimental circuit (necessary measuring instruments are to be incorporated in the circuit).
- b. Construct the experimental circuits in MATLAB/Simulink domain, and simulate it.
- c. Based on the simulation, fill up the Table-2.1 for KVL. Similarly, prepare a table for KCL experiment, and fill it.

| Observation No. | Applied Voltage V (volts) | Voltage across R ₁ (volts) (V ₁) | | Voltage across R ₂ (volts) (V ₂) | | Voltage across R ₃ (volts) (V ₃) | | V ₁ +V ₂ +V ₃ (volts) | |
|-----------------|------------------------------|--|-----------|--|-----------|--|-----------|--|-----------|
| | | Theoretical | Simulated | Theoretical | Simulated | Theoretical | Simulated | Theoretical | Simulated |
| 1 | 100 | | 16.67 | | 33.33 | | 50 | | 100 |
| 2 | 150 | | | | | | | | |
| 3 | 200 | | | | | | | | |
| 4 | 50 | | | | | | | | |

1. F. Assignments:

1. Replace constant voltage source by constant current source with the same magnitude in Fig. 2.a & 2.b, do the simulation again.
2. Replace constant voltage source by variable voltage source (sinusoidal source with the same magnitude, ramp input with slope 1) in Fig. 2.a & 2.b, do the simulation again.
3. Using circuit shown in Fig. 2.c, do the experiment again.

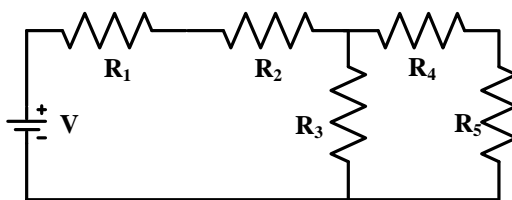


Fig. 2.c