



Roll No.									
----------	--	--	--	--	--	--	--	--	--

## National Institute of Technology Goa

Programme Name: B.Tech., I Sem  
Mid Semester Examinations, February 2021

Course Name: Basic Electrical Science

Date: 03<sup>rd</sup> February 2021

Duration: 1.5 Hours

Course Code: EE151

Time: 9:30 – 11:00 A.M

Max. Marks: 50 Marks


### ANSWER ALL THE QUESTIONS TO THE POINT

#### Section-A

1. Find the equivalent resistance across A and B. Consider the Value of Resistance **as your last digit of Roll No?** [4M]

Note: If your Roll No has last digit 0, consider the value of Resistance as  $1\Omega$

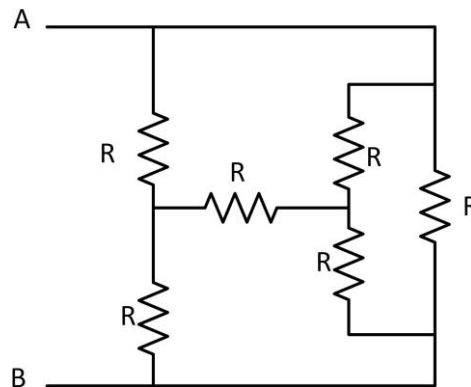Example: Your Roll No is xxxxx2011. Take  $R = 1\Omega$



2.  $-5\text{ C}$  of Charge Contains \_\_\_\_\_ Electrons. [1 M]
3. What will be energy used by battery has to drive  $6.28 \times 10^{18}$  electrons with the potential difference of  $20\text{V}$  across the terminals. [1 M]
4. The conductor material used for House Wiring is \_\_\_\_\_ [1 M]
5. Superconductivity Temperature is \_\_\_\_\_ [1 M]
6. A  $60\text{W}$  bulb is kept on for 12 hours. How many units of energy is Consumed by it? What is the bulbs resistance if it is connected across  $230\text{ V}$  Supply? [2 M]
7. For a given  $80\text{ Hz}$  AC System frequency, what is the time duration of each cycle? [1 M]

## Section-B

8. Calculate the resistance between A and B points in the network. Fig.2.7.

[6 M]


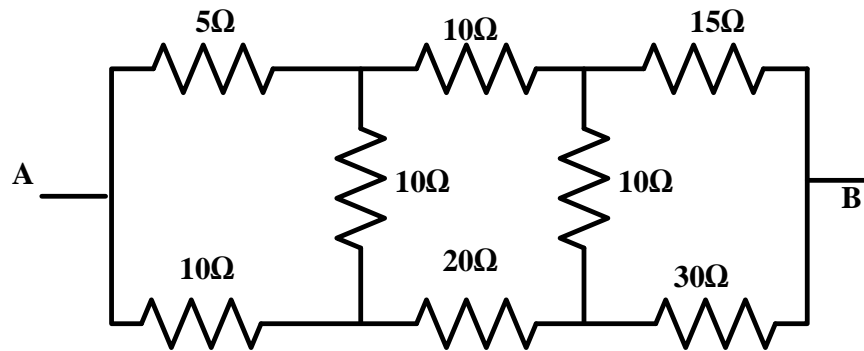


Fig.2.7.

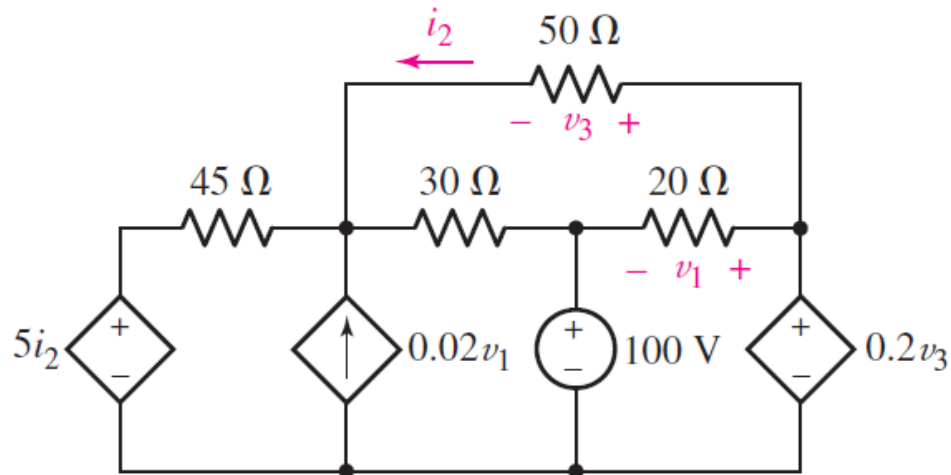9. For the Figure below, write only the simultaneous equations that must be solved to determine voltages  $v_1$  and  $v_3$  using (a) nodal analysis; (b) mesh analysis. [4M X 2]



10. Find the Thevenins equivalent of the following circuit across AB in Fig.3

[6 M]

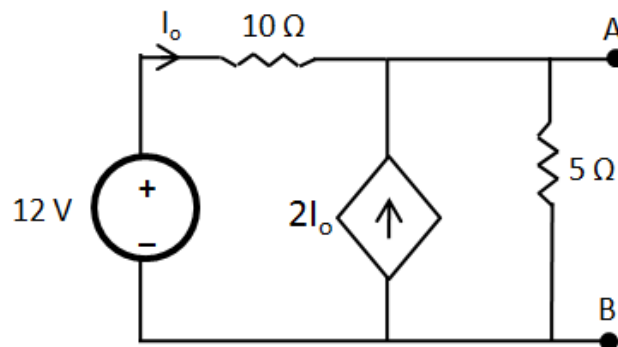


Fig. 3

11. Using nodal analysis, find the voltages  $V_A$ ,  $V_B$  and  $V_x$ , in which  $I_1 = 0.4 \text{ A}$

[7 M]


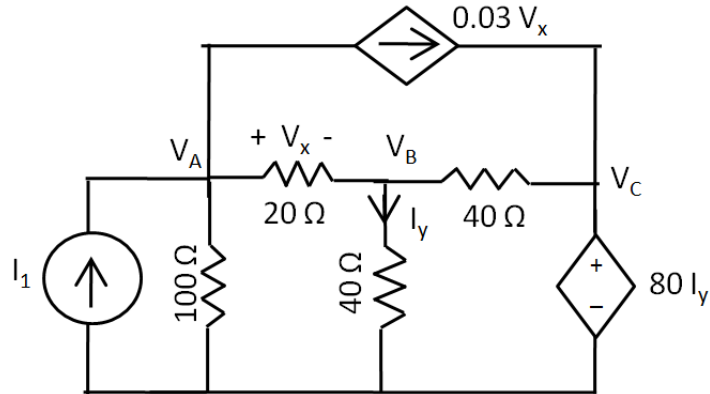


Fig. 4.

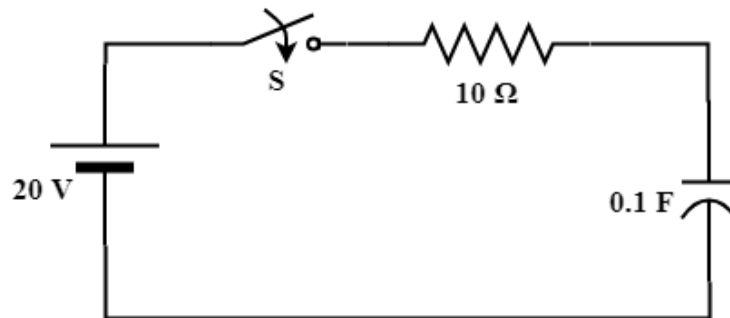12. For the RC circuit shown below switch is closed at  $t = 0 \text{ sec}$ . Find

- The current expression in the circuit and its value at  $t = 0^+$ ? [2 M]
- Value of current after 2 time constants? [2 M]
- The voltage expression across capacitor and resistor? (Initial charge in storage elements is zero) [2 M]
- Value of Voltage across capacitor and resistor after 3 time constants? [2 M]
- The power expression across capacitor and resistor? [2 M]
- Plot the Voltage and Current variation across time with free hand. [2 M]



\*\*\*\*\*